

Questions?

- Project?

Show and tell


Introduction to electronics

- Based on “Practical Electronics for Inventors” by P. Scherz
 - All the drawing and sketches are from this book
- Today
 - Overview of the key components
 - Simple circuits design



Resistor: key facts

$$V = RI$$



$$I = \frac{V}{R}$$

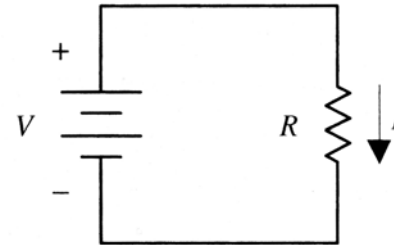

$$R_{eq} = R_1 + R_2$$

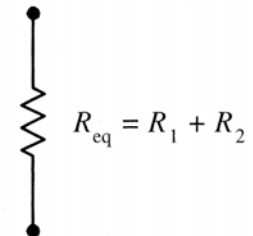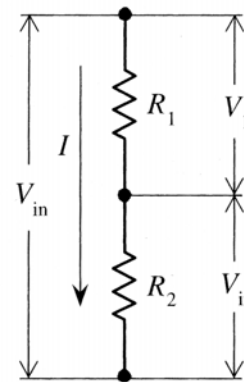

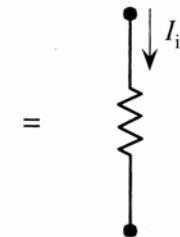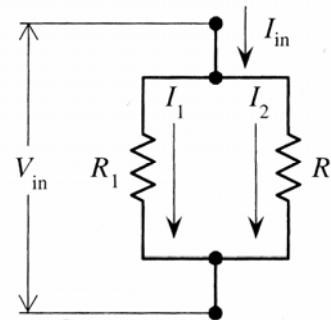
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$




$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

Resistor: Examples


RESISTOR COLOR CODE GUIDE

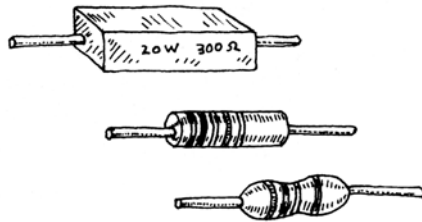


Fixed Resistors

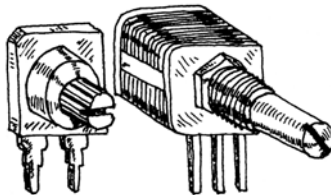


Potentiometers and Trimmers

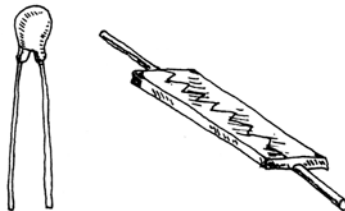


Thermistors and Phototransistors

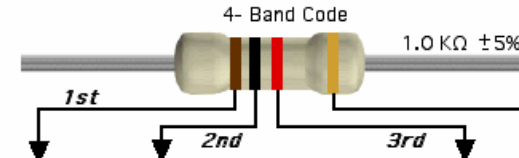

Color	1st Band	2nd Band	3rd Band	Decimal Multiplier		Tolerance
Black	0	0	0	1	1	
Brown	1	1	1	10	10	± 1 %
Red	2	2	2	100	100	± 2 %
Orange	3	3	3	1K	1,000	
Yellow	4	4	4	10K	10,000	
Green	5	5	5	100K	100,000	
Blue	6	6	6	1M	1,000,000	
Violet	7	7	7	10M	10,000,000	
Gray	8	8	8		100,000,000	
White	9	9	9		1,000,000,000	
Gold				0.1		± 5 %
Silver				0.01		± 10 %
None						± 20 %

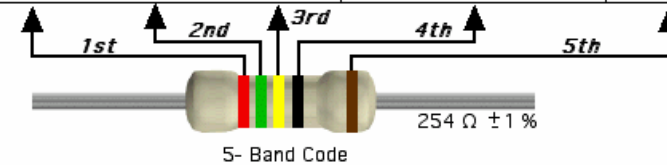

Calculation

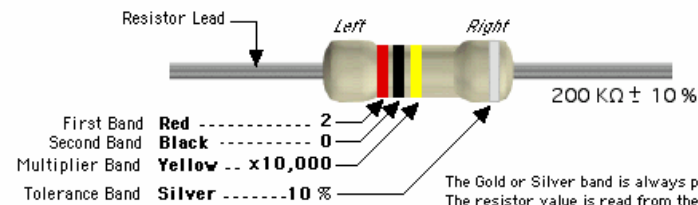

Equation

$$20 \times 10,000 = 200,000$$



$$1,000 = 1K$$

Resistor = 200 KΩ
with a ± 10 % Tolerance



If there is no tolerance band, then find the side that has a band closest to a lead and make that the first band.

Resistor: Key circuits

- Load limiting

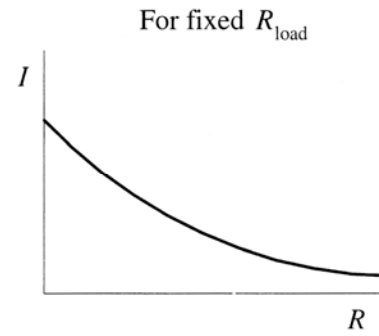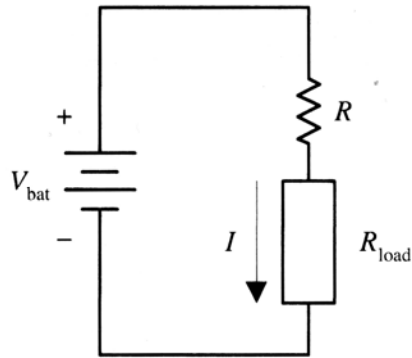


- Voltage control

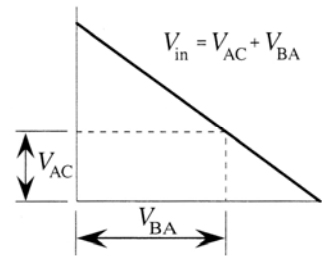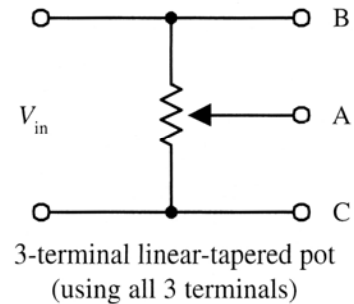

Capacitor: key facts


$$I = C \frac{\partial V}{\partial t}$$

$$\partial V = \frac{I}{C} \partial t$$

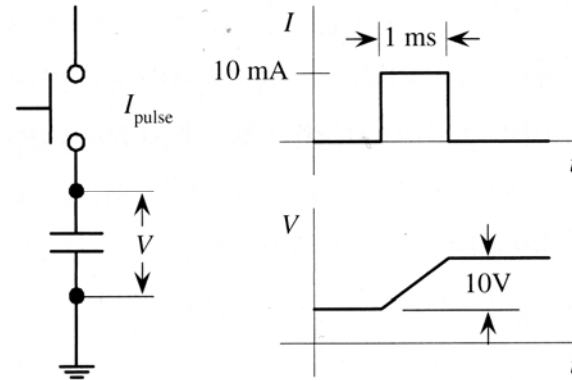


$$C = 1 \mu\text{F}$$

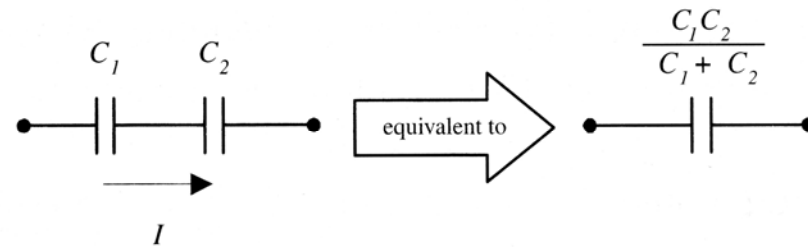
$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2}$$




$$C_{\text{eq}} = C_1 + C_2$$

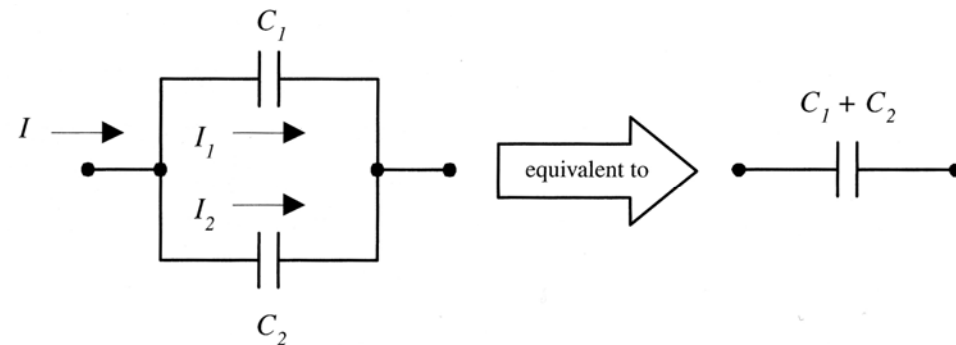



Capacitor: Examples

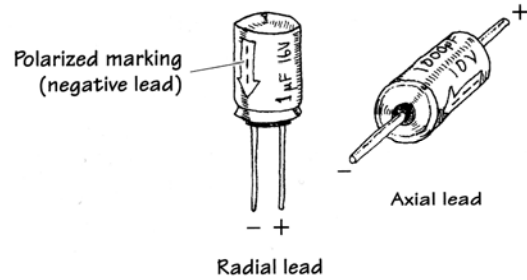


Electrolytic

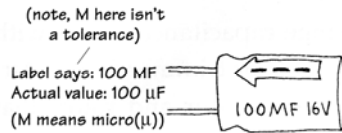


Tantalum

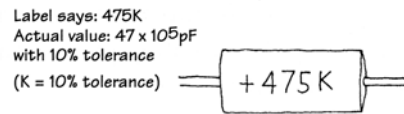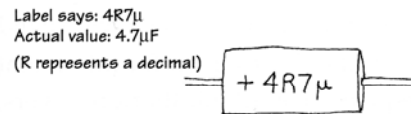


Dipped Tantalum

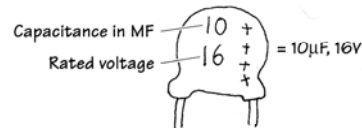




Mylar

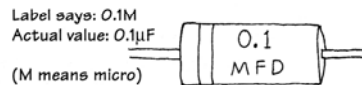

Standard

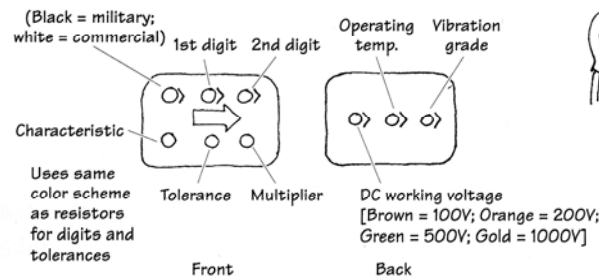

Ceramic

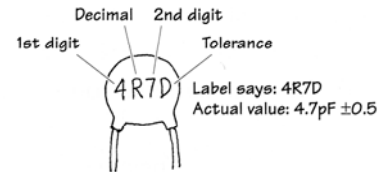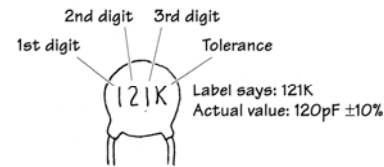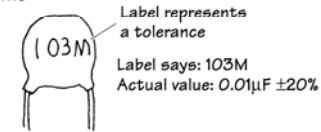

European Marking




Multipliers

- O = none
- 1 = × 10
- 2 = × 100
- 3 = × 1000
- 4 = × 10,000

Tolerance





- Z = +80%, -20% (asymmetric capacitor construction)
- M = ±20%
- K = ±10% B = ±0.1%
- J = ±5% A = ±0.05%
- G = ±2%
- F = ±1%
- D = ±0.5%
- C = ±0.25%
- B = ±0.1%
- A = ±0.05%

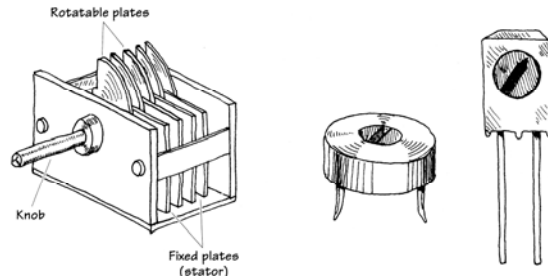- 1pF = 1 × 10⁻¹²F
- 1nF = 1 × 10⁻⁹F
- 1μF = 1 × 10⁻⁶F




Capacitor: Key circuits

- Filtering

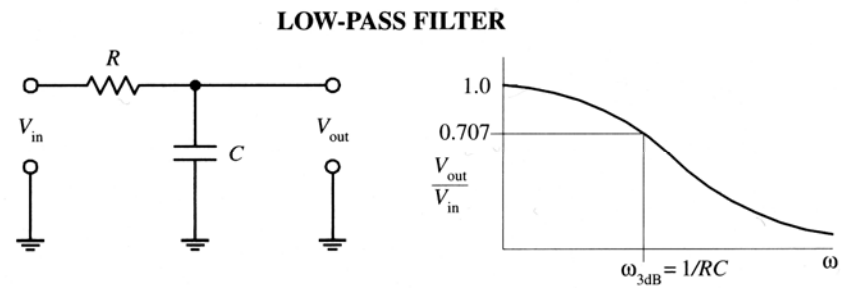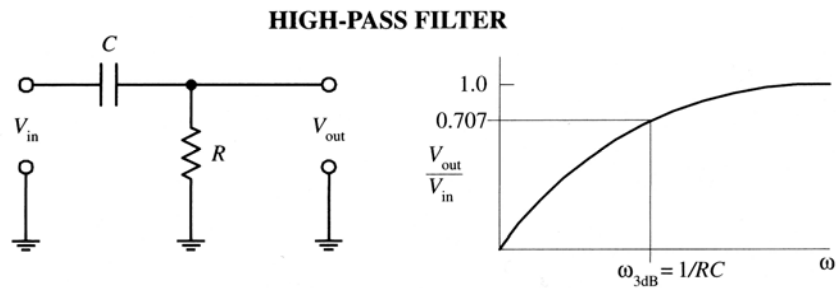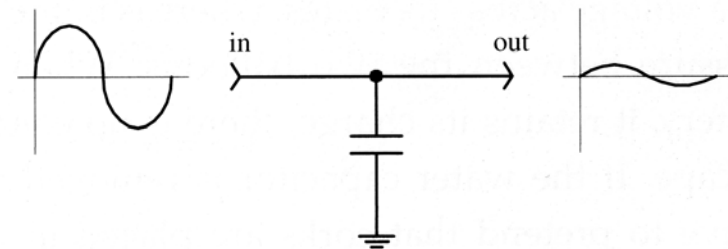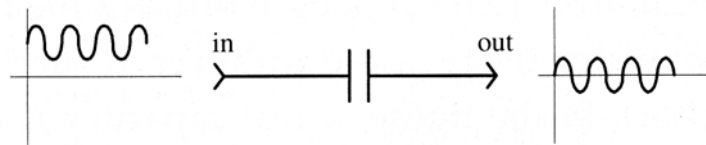


Capacitor: Key circuits (II)

- Low-pass filter

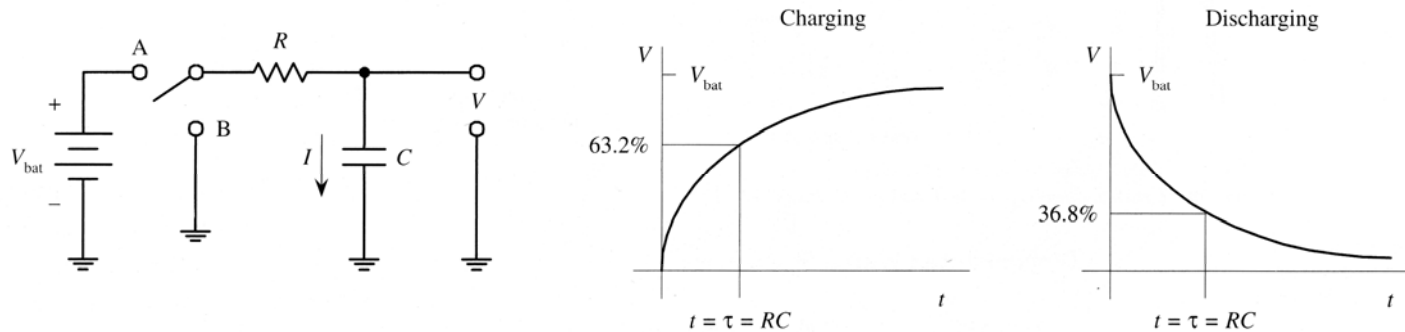


Power Supply Filtering

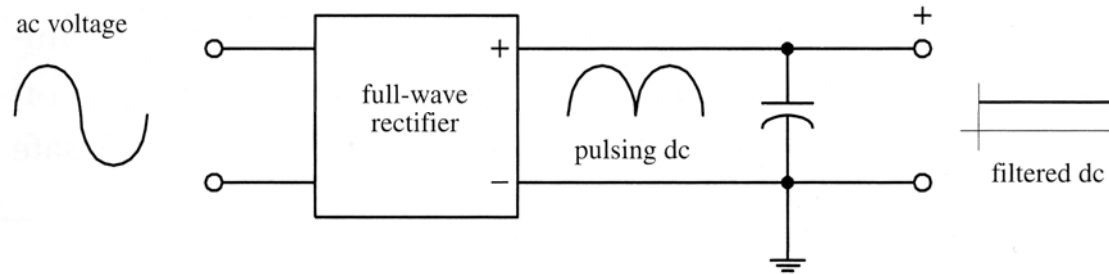

Be careful about discharge



Spike and Noise Suppression

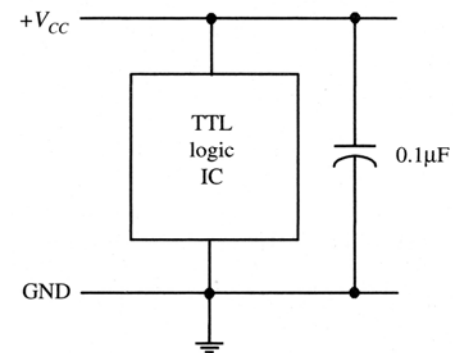


Inductor: key facts

$$V = L \frac{\partial I}{\partial t}$$


$$\partial I = \frac{V}{L} \partial t$$

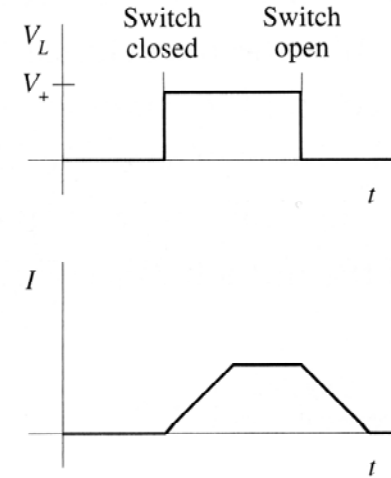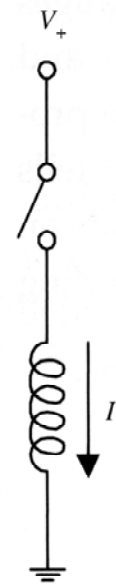

$$L_{eq} = L_1 + L_2$$



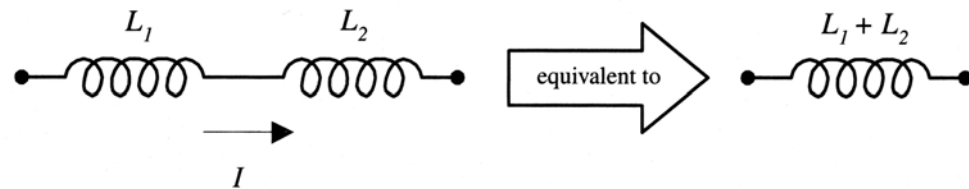

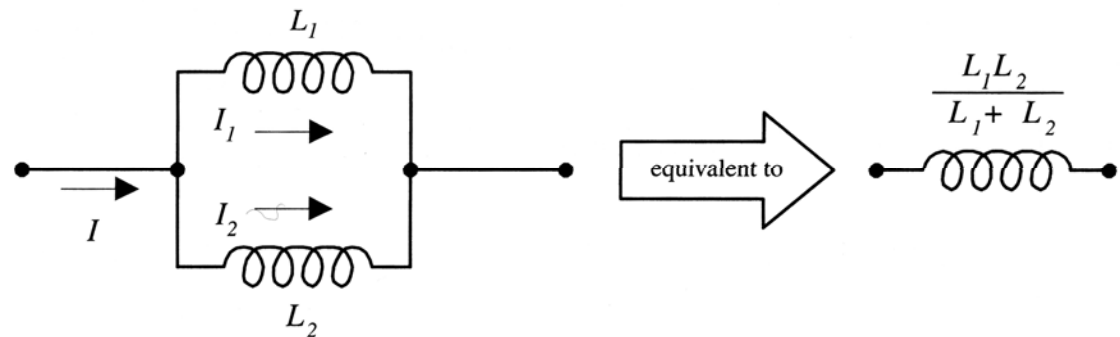
$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$$




Inductor: Examples


Chokes

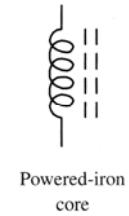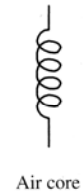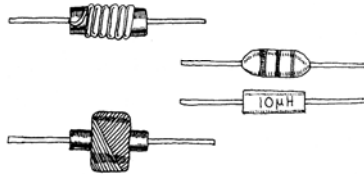








Subminiature Relays

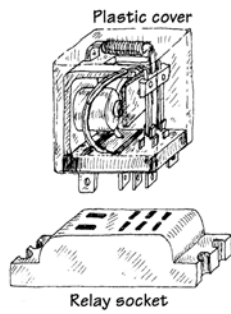

Miniature Relays

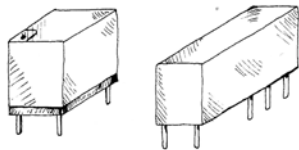


Mechanical Relay

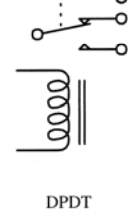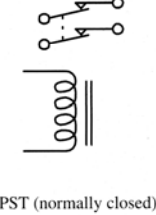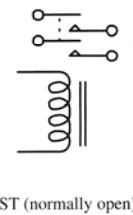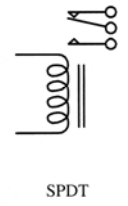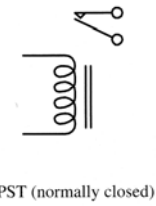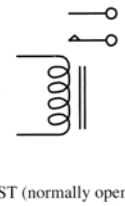
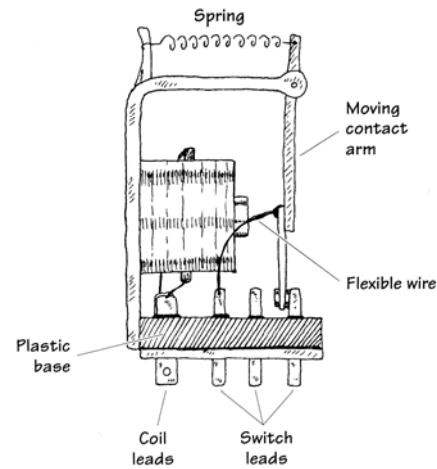


Inductor: Key circuits

- Filtering


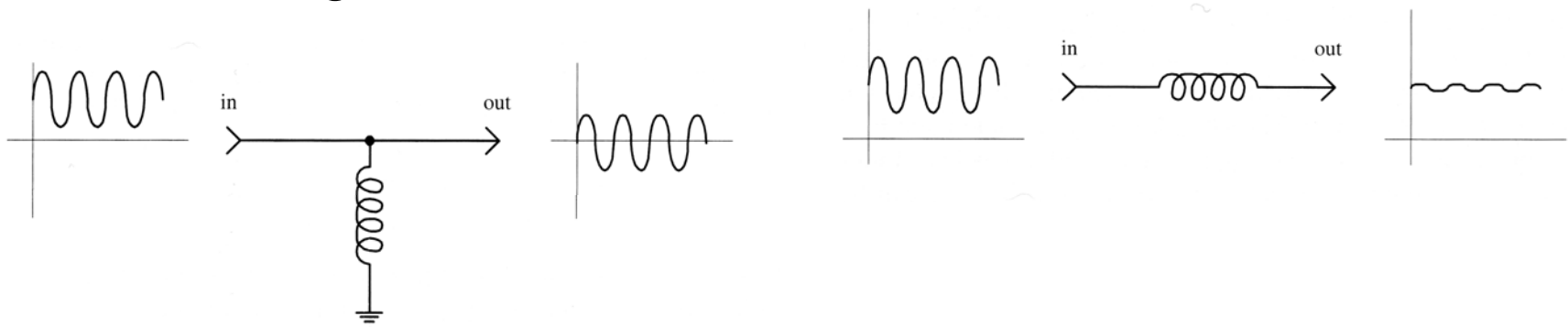


- Spike

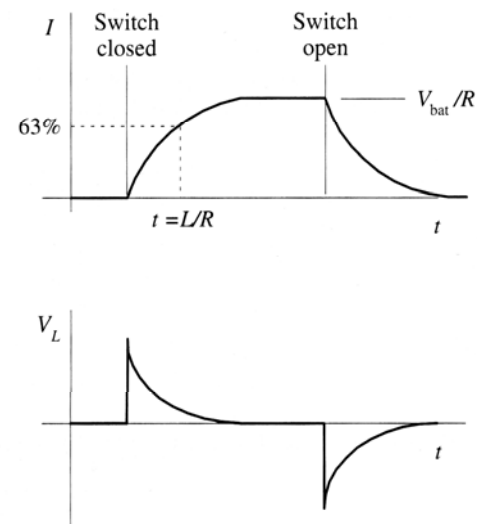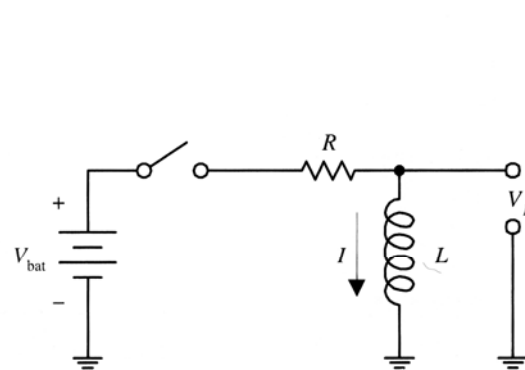

Diode: key facts

- Unidirectional conduction

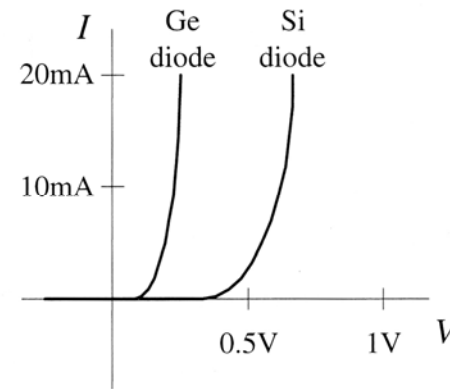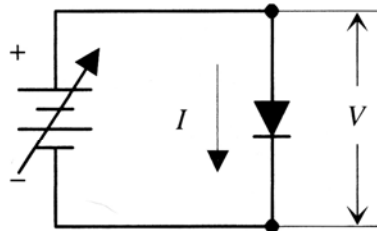

- Examples


Glass-encapsulated signal diode



Plastic-encapsulated diode




Power rectifier

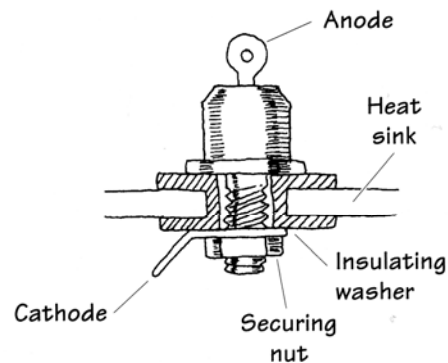


Diode: Key circuits

- Rectifier



Half-Wave Rectifier

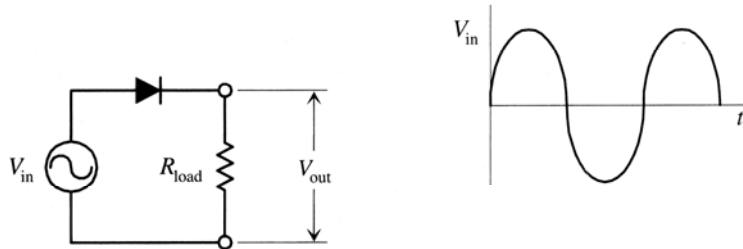

Full-Wave Bridge Rectifier

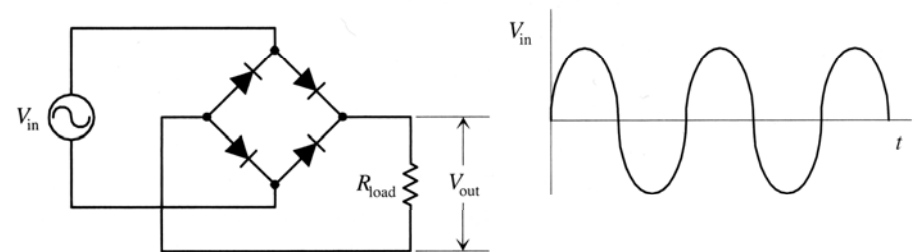

Basic AC-to-DC Power Supply

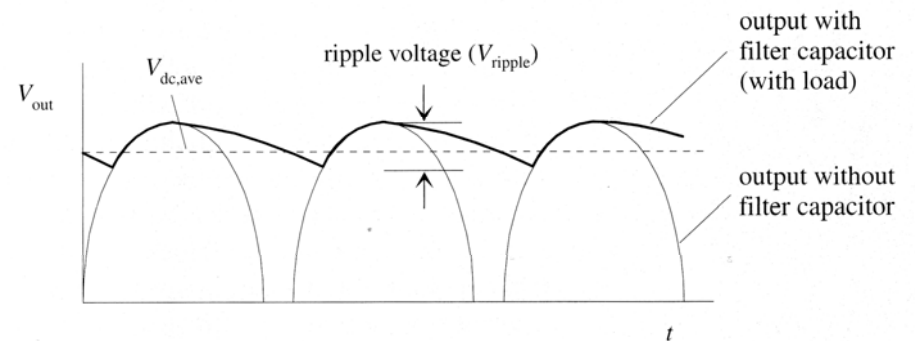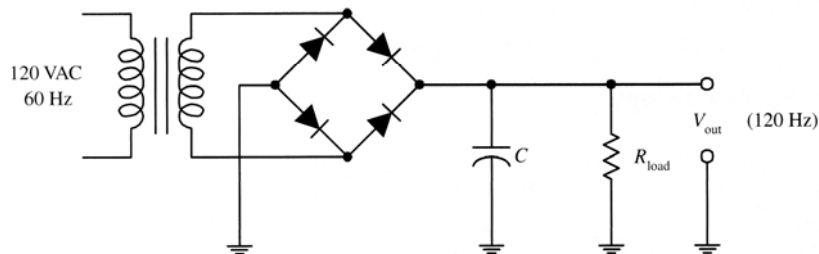

Diode: Key circuits (II)

- Spike suppressor


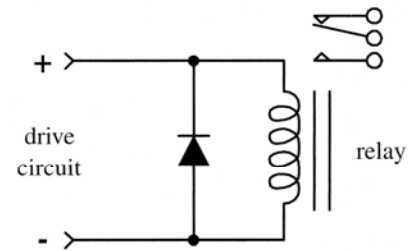


FIGURE 4.14 (Continued)

- Voltage regulator

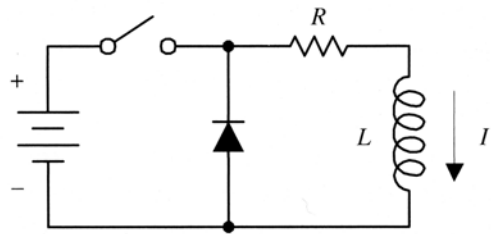