
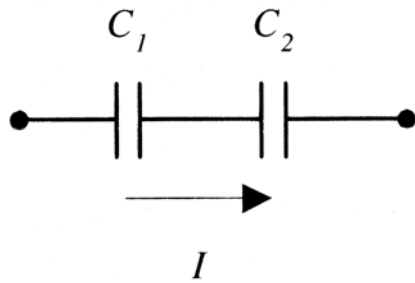
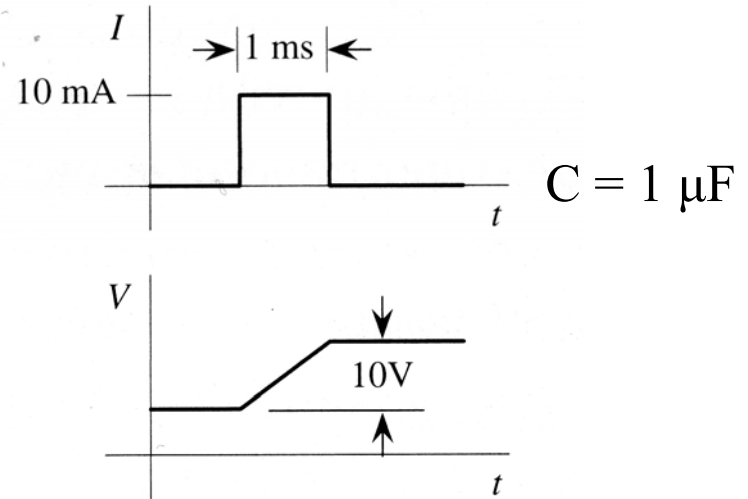


Questions?


- Show and tell?
- Project?

Capacitor: key facts
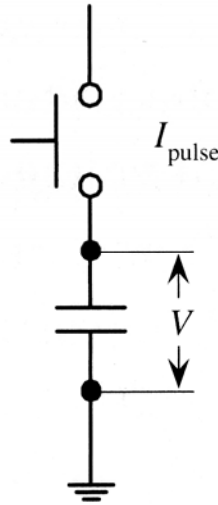
$$I = C \frac{\partial V}{\partial t}$$
$$\partial V = \frac{I}{C} \partial t$$



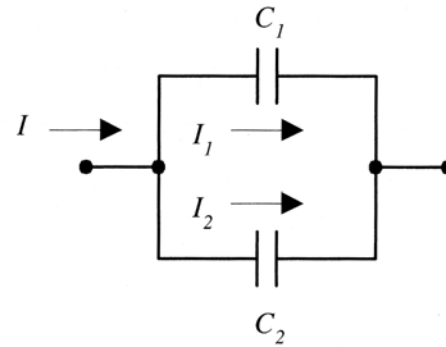
$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2}$$




$$C_{\text{eq}} = C_1 + C_2$$



Capacitor: Examples

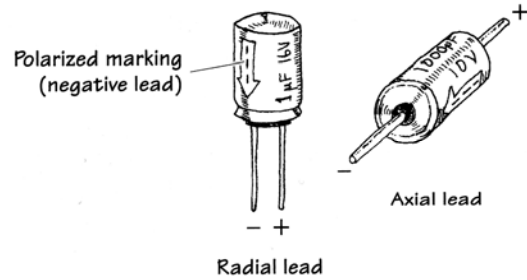


Electrolytic

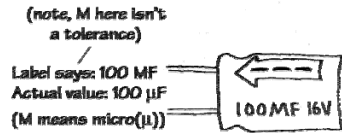


Tantalum

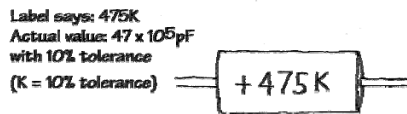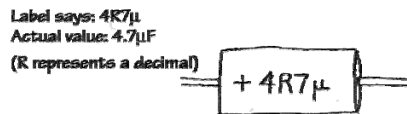


Dipped Tantalum

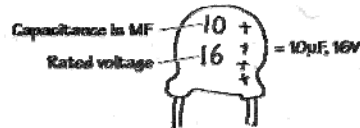




Mylar

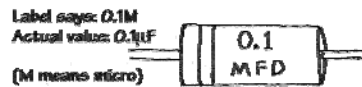

Standard

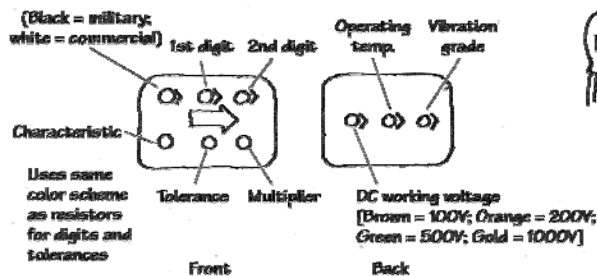

Ceramic

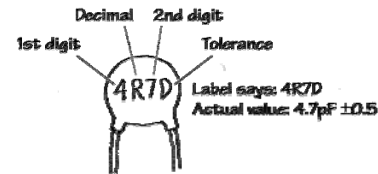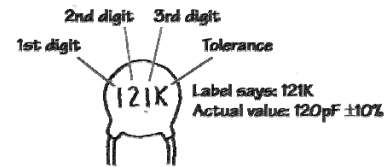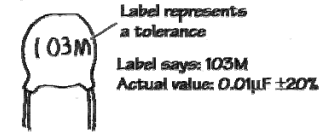

European Marking



Multipliers




- 0 = none
- 1 = x 10
- 2 = x 100
- 3 = x 1000
- 4 = x 10,000

Tolerance




- Z = +20%, -20% (asymmetric capacitor construction)
- M = \pm 20%
- K = \pm 10% B = \pm 0.1%
- J = \pm 5% A = \pm 0.05%
- G = \pm 2%
- F = \pm 1%
- D = \pm 0.5%
- C = \pm 0.25%
- B = \pm 0.1%
- A = \pm 0.05%

- 1pF = 1 x 10⁻¹²F
- 1nF = 1 x 10⁻⁹F
- 1 μ F = 1 x 10⁻⁶F


Capacitor: low pass filter (I)

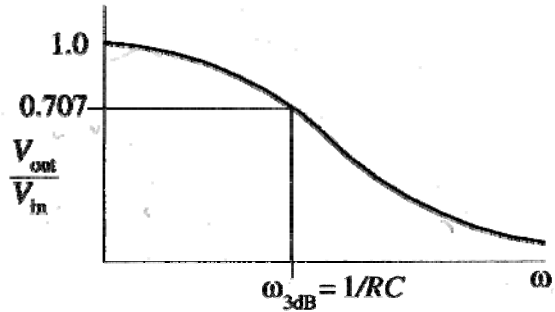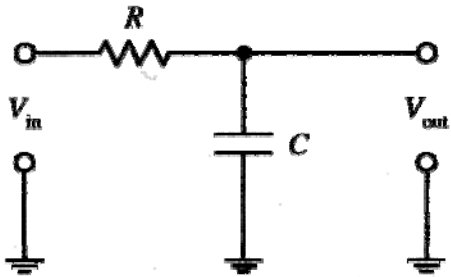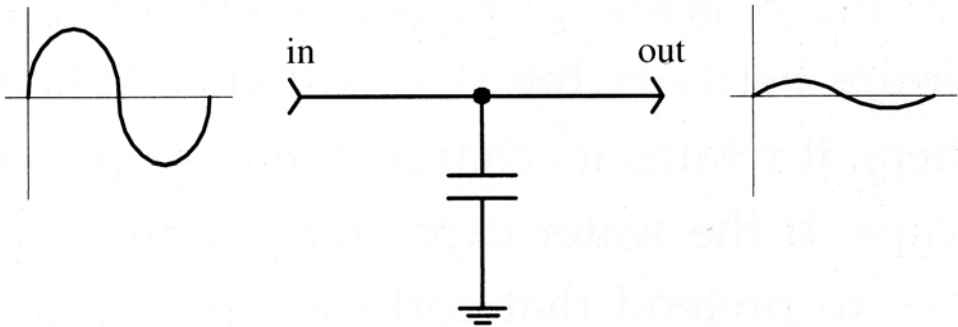

Capacitor: low pass filter (II)

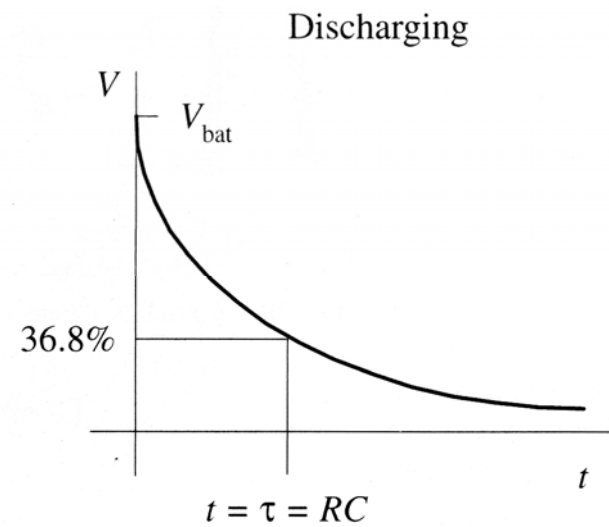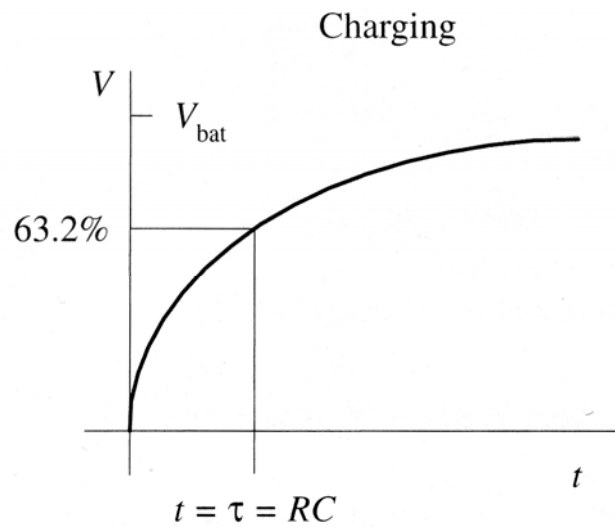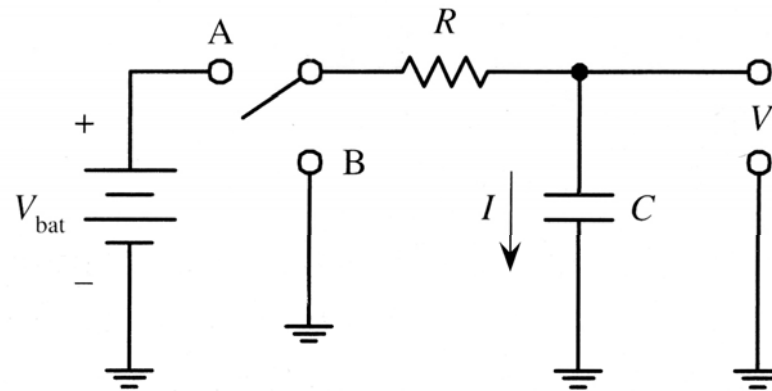


Capacitor: low pass filter (de-bouncing)

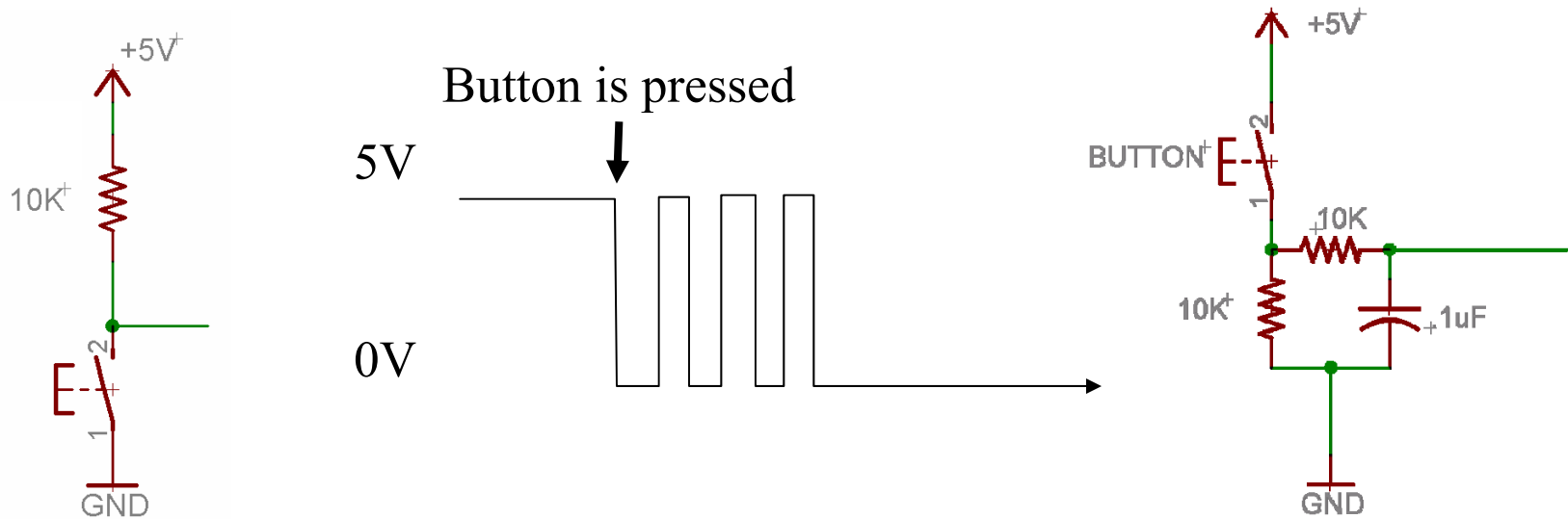

- Work in conjunction with Schmitt Trigger input (such as port RE1)
- Software solution: wait until the end of the bouncing.


Capacitor: low pass filter (power)

Power Supply Filtering



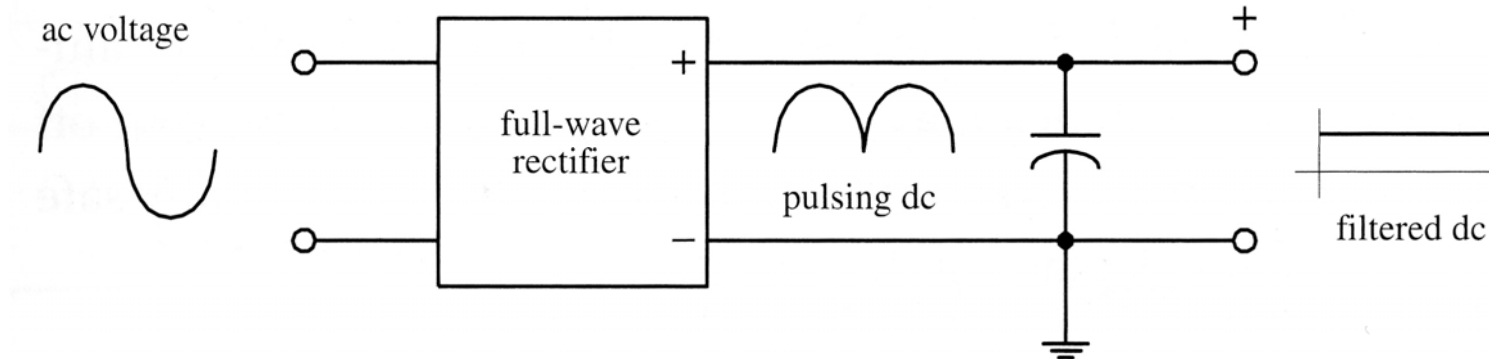


Be careful about discharge


Spike and Noise Suppression

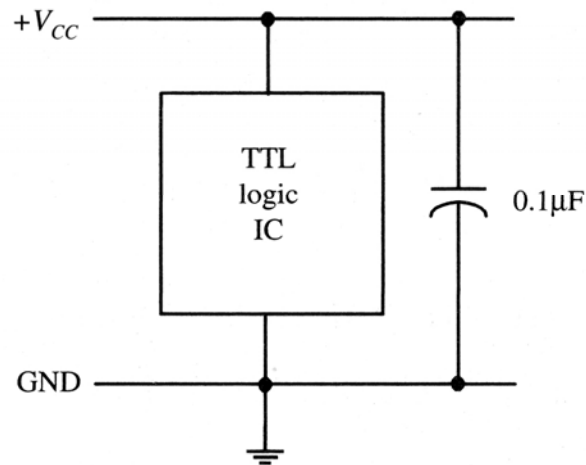


Capacitor: high pass filtering

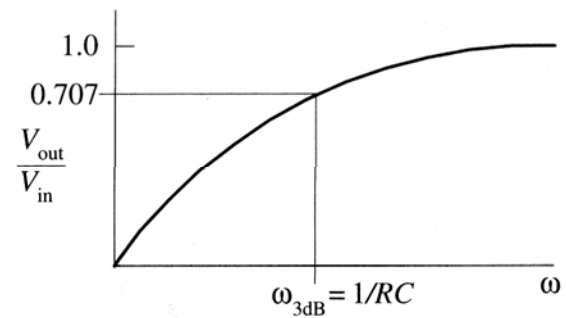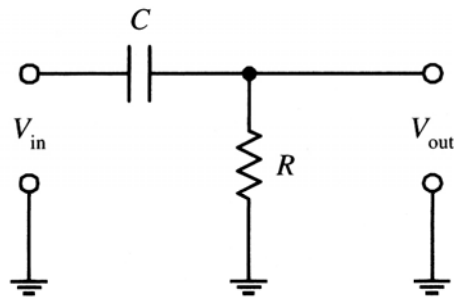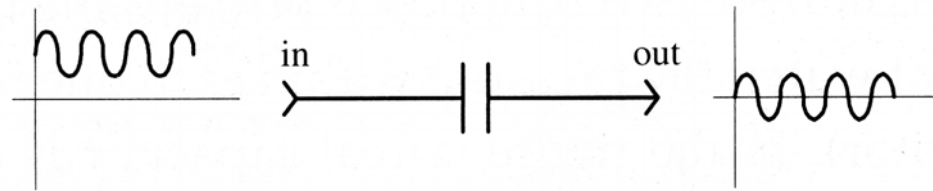


Operational Amplifier: key facts

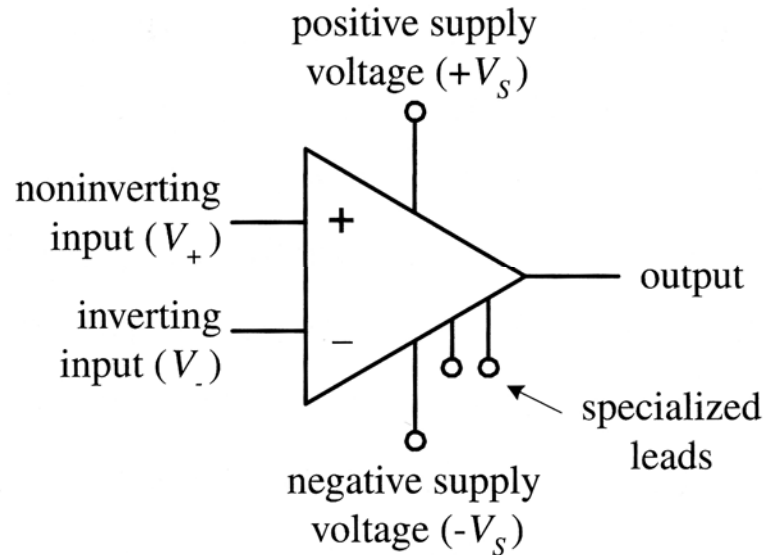

Ideal op amp


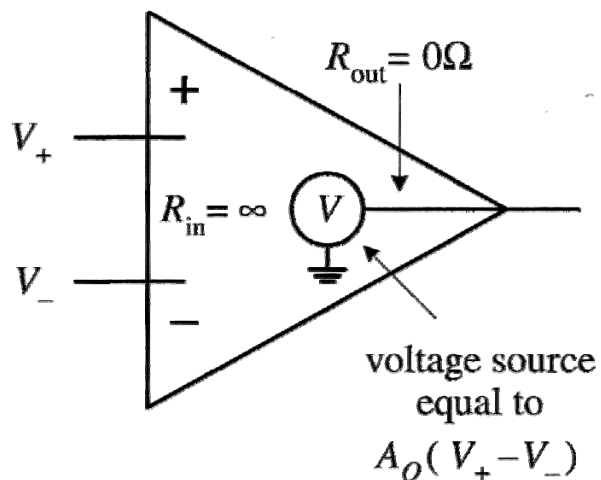


Real op amp


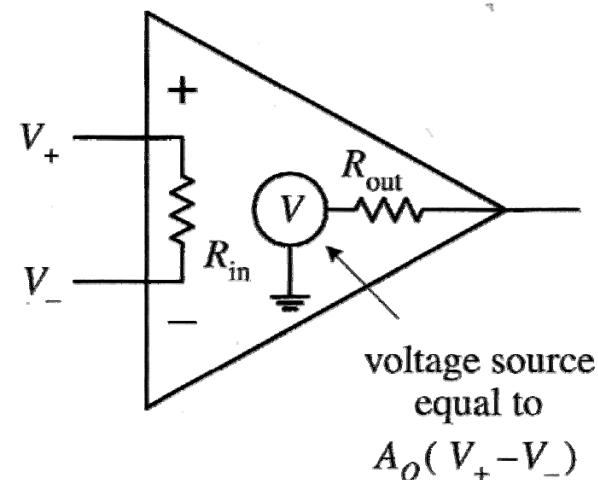


Operational Amplifier: key facts



Noninverting setup

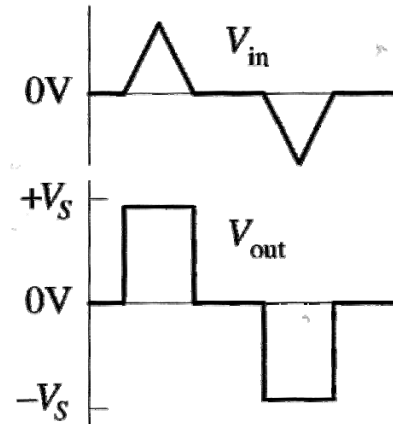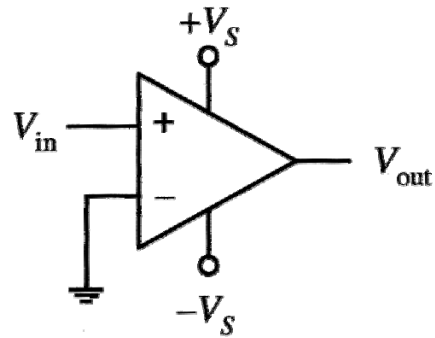


Inverting setup

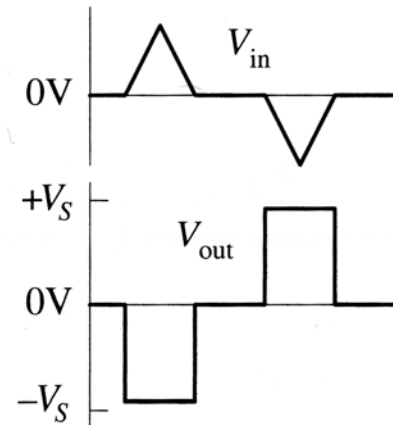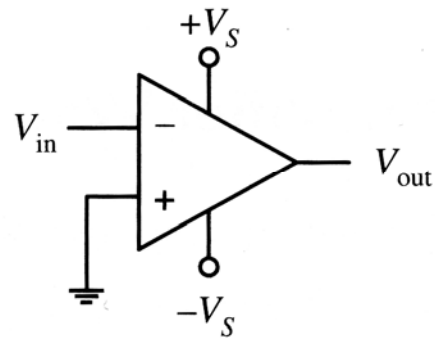


Operational Amplifier: Examples

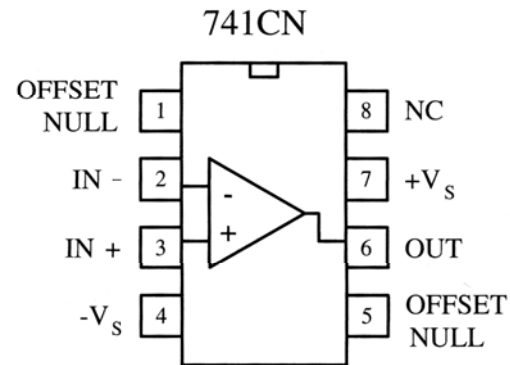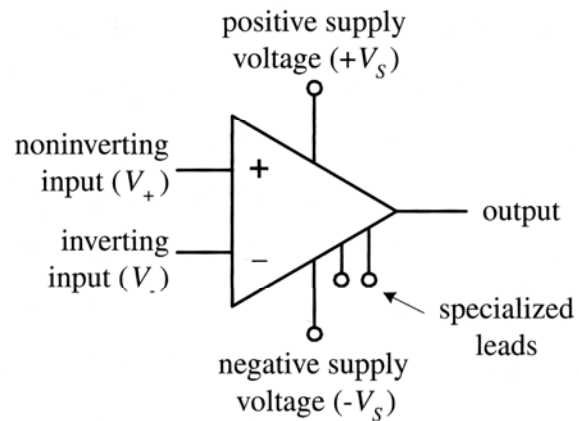

Audio Amplifiers

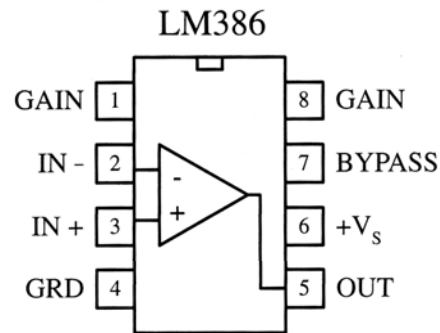


low-voltage power amplifier

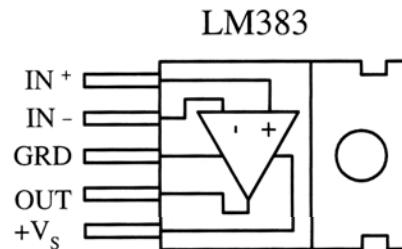



8-watt power amplifier

Operational Amplifier: Key circuits

- Follower

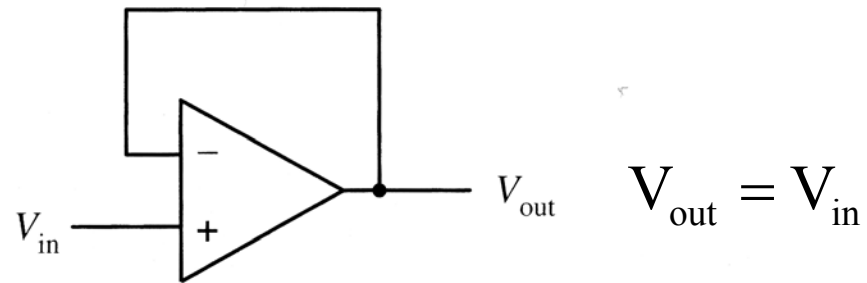


- Inverting amplifier

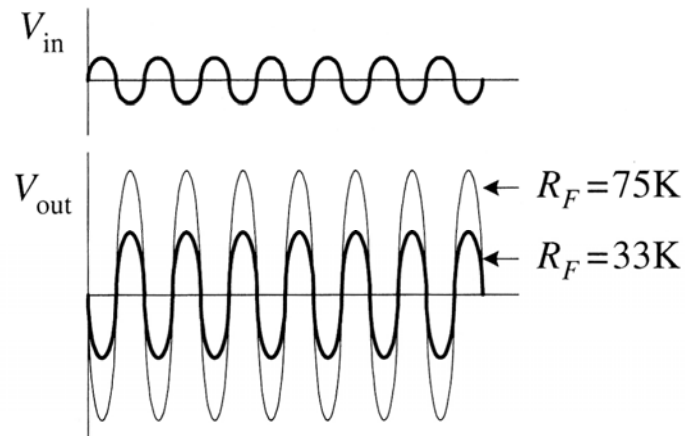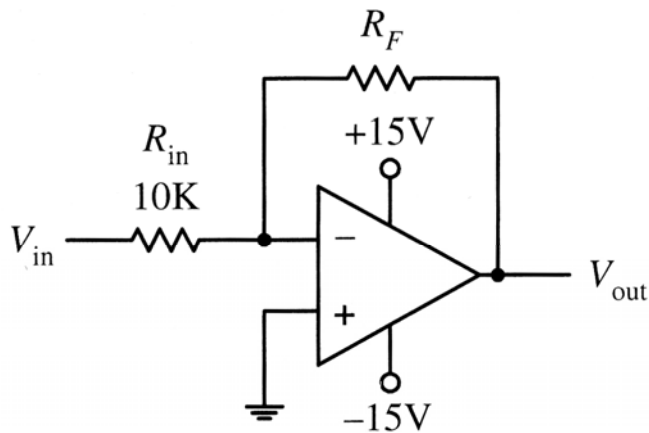

$$V_{out} = -\frac{R_F}{R_{in}} V_{in}$$

Operational Amplifier: Key circuits



- Amplifier

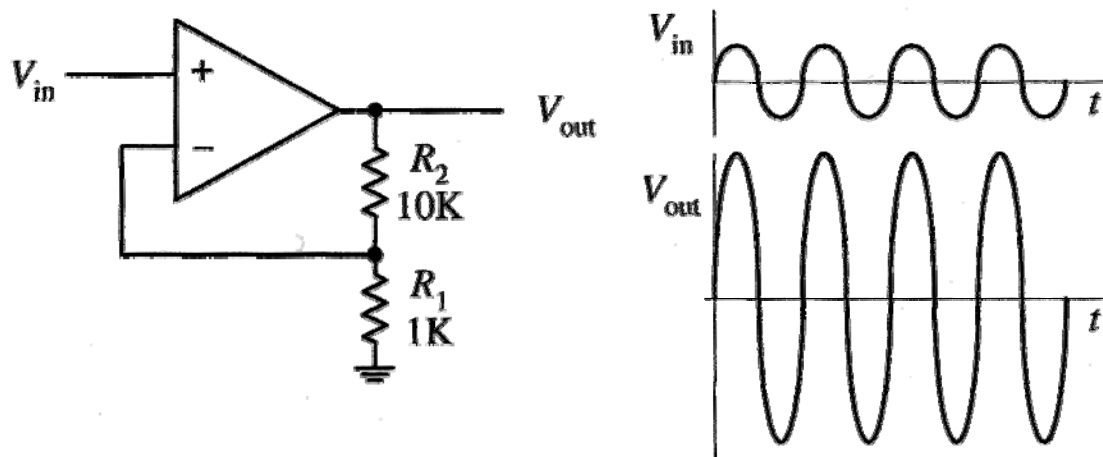

$$V_{out} = \frac{R_1 + R_2}{R_1} V_{in}$$

Operational Amplifier: Key circuits


- Adder

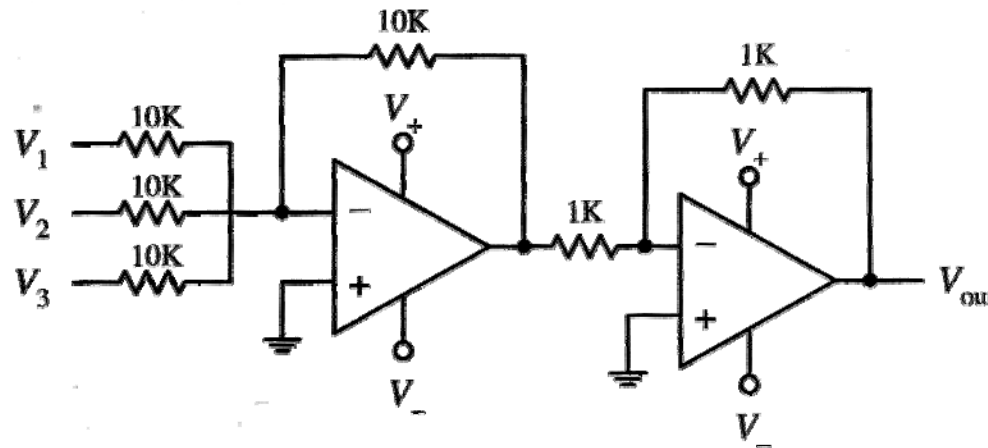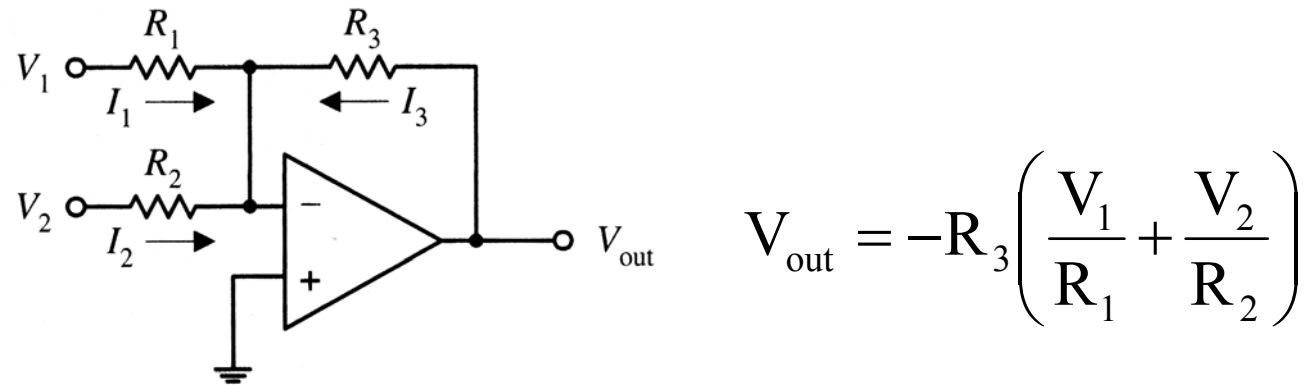


- Other operations are possible
 - Addition, derivation, integration

Operational Amplifier: Key circuits



- Power supply

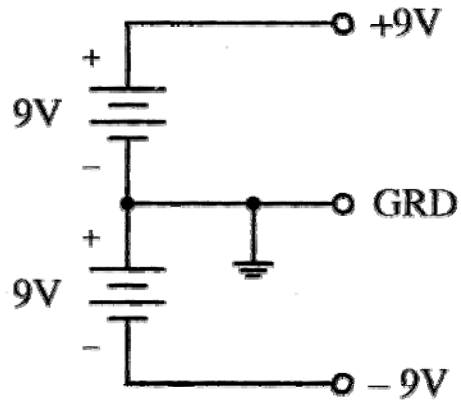

Reverse-polarity protection

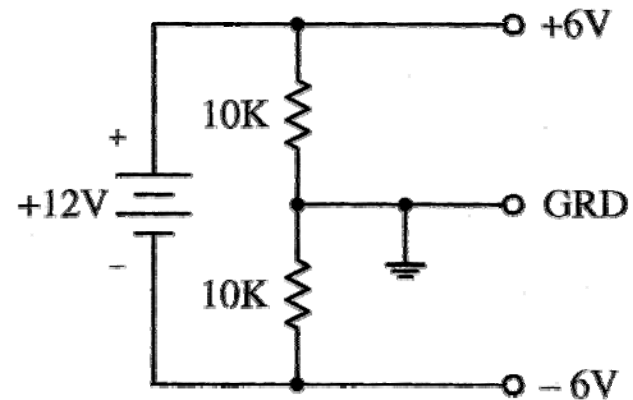


Oscillation prevention

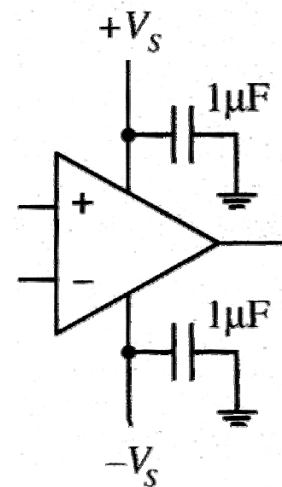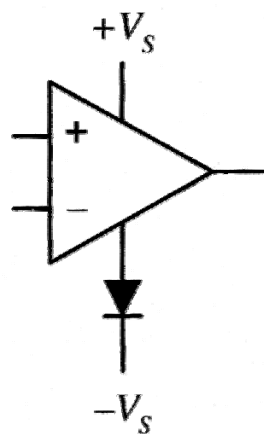

Operational Amplifier: Key circuits

Noninverting single-supply ac amplifier

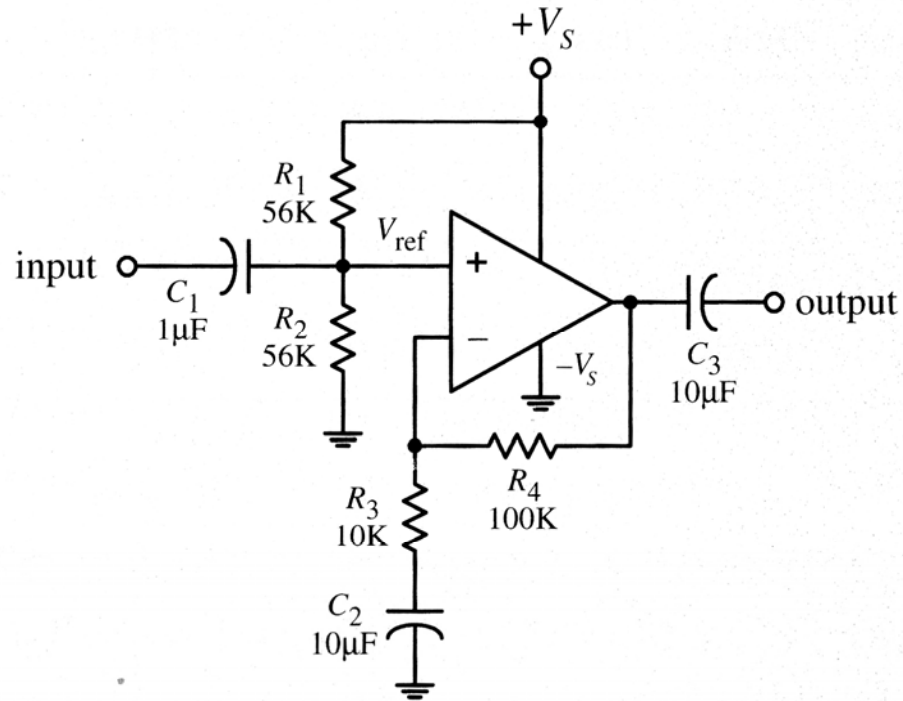

Inverting single-supply ac amplifier

