

Honors Homework 2

Morally Due Mon Feb 14 at 9:00 AM. Dead Cat Feb 16 at 9:00 Am
COURSE WEBSITE:

<http://www.cs.umd.edu/~gasarch/COURSES/752/S22/index.html>
(The symbol before gasarch is a tilde.)

1. (20 points) Consider the following table

| X | Y | Z | Output |
|---|---|---|--------|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

- (a) (10 points) Draw the k-map for the table.
(b) (10 points) Give the simplified expression from the k-map.

2. (30 points) Consider the following table

| X | Y | Z | Output |
|---|---|---|--------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

- (a) (10 points) Draw the k-map for the table.
(b) (10 points) Give the simplified expression from the k-map.
(c) (10 points) Give the expression in terms of exclusive-or.

3. (20 points) Consider the following table

| W | X | Y | Z | Output |
|---|---|---|---|--------|
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 |

(a) (10 points) Draw the k-map for the table.

(b) (10 points) Give the simplified expression from the k-map.

4. (10 points) In recitation, the SR Latch was made up of two NOR Gates. Draw an SR Latch with NAND and NOT gates.
5. (10 points) When $D = 1$ and the clock = 0 what does the clocked D latch produce?
6. (10 points) How many AND gates are in a 16-bit register made up of flip-flops?