

Truth Values and Bits

Standard Convention: TRUE is 1, FALSE is 0

Standard Convention: n -inputs viewed as n -bit number.

Prop Formula is now **Boolean Formula**

Redo TTs

Basic Gates

Definition

- ① *AND GATES*: k Inputs and outputs AND of them.
- ② *OR GATES*: k Inputs and outputs OR of them.
- ③ *XOR GATES*: k Inputs and outputs XOR of them.
- ④ *NOT GATES*: 1 Inputs and outputs NEG of it.
- ⑤ Such devices **really** exist!
- ⑥ Draw on board.

Why AND, OR, XOR?

Discuss why Gates for AND, OR, XOR?

What is a Circuit?

Definition

A **Circuit** has n Boolean Inputs which feed into gates and at the end have one or more outputs.

Do Examples

Building a Circuit for a 1-Bit Adder

Definition

A *1-Bit Adder* is a circuit that takes 2 bits and outputs their sum (which will be 2 bits).

Make TT for 1-bit Adder

New Problem

- ❶ Old Problem: Given a Fml, find the TT for it.
- ❷ New Problem: Given a TT, find a Fml for it.
- ❸ New Problem: Given a Fml, find a Circuit for it.
(Easy)

Given a TT...

- 1 For each row R of the TT that returns 1 (or T):
For each variable x_i
 $L_i = x_i$ if Row R has $x_i = T$;
 $L_i = \neg x_i$ if Row R has $x_i = F$.
- 2 Write down mini-fml $L_1 \wedge \dots \wedge L_n$
KEY: This mini-fml is true IFF that row happens.
- 3 Output the OR of all of the minifmls.

Do Example

The 3-Bit Adder...

We do the following

- 1 Write a TT for a 3-bit adder. Input is a 3-bit number **in base 2**.
- 2 Write a formula for the 4-outputs of a 3-bit adder.
- 3 Draw a circuit for the 3-bit adder
- 4 Easy to generalize?

Half-Adders and Full-Adders...

Definition

- 1 A *Half Adder (HA)* is a circuit that has 2 boolean inputs, 2 boolean outputs, and outputs the sum and the carry.

Get Circuit For a HA

- 2 A *Full Adder (FA)* is a circuit that has 3 boolean inputs, 2 boolean outputs, and outputs the sum and the carry.

Get Circuit For a FA

Using HA's and FA's build an n -bit Adder