

CMSC 311
Solutions to Midterm II

Problem 1.

```

add  $s0, $zero, $zero # $s0 = 0; counts number of 28's
lw   $s2, 240($zero)  # $s2 = length of array
beq  $s2, $zero, done # if array length = 0 then done
sll  $s2, $s2, 2       # multiply array length by 4 to obtain number of bytes
lw   $s1, 236($zero)  # $s1 = starting address of array
add  $s3, $s0, $s1    # $s3 is address after last number in array
addi $s4, $zero, 28   # $s4 = 28 is number being searched for
loop: lw  $t1, 0($s0)  # load next number in array
      bne $t1, $s4, skip # skip if number ≠ 28
      addi $s0, $s0, 1 # increment number of 28's
skip: addi $s1, $s1, 4 # address of next number in array
      bne $s1, $s3, loop # loop if next address still in bounds
done: sw  $s0, 244($zero) # store number of 28's

```

NOTE: Instead of

```

bne  $t1, $s4, skip # skip if number ≠ 28
addi $s0, $s0, 1   # increment number of 28's

```

we could use the *pseudo-instruction*

```

seq  $t2, $t1, $s4 # $t2 is set to 1 if number is 28; 0 otherwise
add  $s0, $s0, $t2 # increment number of 28's if number equals 28

```

The seq pseudo-instruction substitutes two MIPS instructions for the one bne instruction, but avoids a potential branch.

Problem 2. The routine splits \$s2 into left and right halves. A pair of bits are peeled off the right ends of the two halves, one from each. The pair of bits are pasted into the result \$s1. In preparation for the next pair of bits, the two halves are each shifted right one bit position and \$s1 is rotated right two bit positions.

```

andi $s1, $zero, $zero # initialize $s1 to 0
andi $t1, $s2, 216 - 1 # $t1 is right half of $s2
srl  $t0, $s2, 15      # $t0 is left half of $s2 shifted left 1 bit
addi $t5, $zero, 16   # counter for number of passes
loop: andi $t2, $t1, 2 # get next bit of left side (from right to left)
      or   $s1, $s1, $t2 # put bit into result
      andi $t2, $t0, 1 # get next bit of right side (from right to left)
      or   $s1, $s1, $t2 # put bit into result
      srl $t1, $t1, 1   # shift down bits of left side
      srl $t0, $t0, 1   # shift down bits of right side
      ror $s1, $s1, 2   # prepare for next two bits; pseudo-instruction
      addi $t5, $t5, -1 # decrement counter
      bne $t5, $zero, loop

```

Problem 3. Form the three values

$$\overline{x_0 \oplus x_1} \quad \overline{x_1 \oplus x_2} \quad \overline{x_2 \oplus x_3}$$

Use them as inputs to a 3×1 multiplexer selected by $i_1 i_0$.

$$a \oplus b = a \bar{b} \vee \bar{a} b$$

So $\overline{a \oplus b}$ needs two AND gates and a NOR gate.

A 3×1 multiplexer needs three AND gates and an OR gate.

Problem 4. We need two bits to control the inputs to the shift register. We can use the leftmost bit, call it L , in the shift register as one control bit: The output L will be 0 until the leftmost 1 shifts into the leftmost position at which point it will be 1 for exactly one clock cycle. The final right shift will make L 0 again (forever).


A T flip-flop with input from L will stay 0 until one clock cycle after L flips to 1, and then stay 1 (forever).

The following table gives the necessary inputs $i_1 i_0$ for the shift register given the outputs of L and of the T flip-flop, which we call Q .

L	Q	i_1	i_0
0	0	1	0
1	0	0	1
0	1	0	0


Using minterms, we get

$$i_1 = \bar{L} \bar{Q} \quad i_0 = L \bar{Q}$$

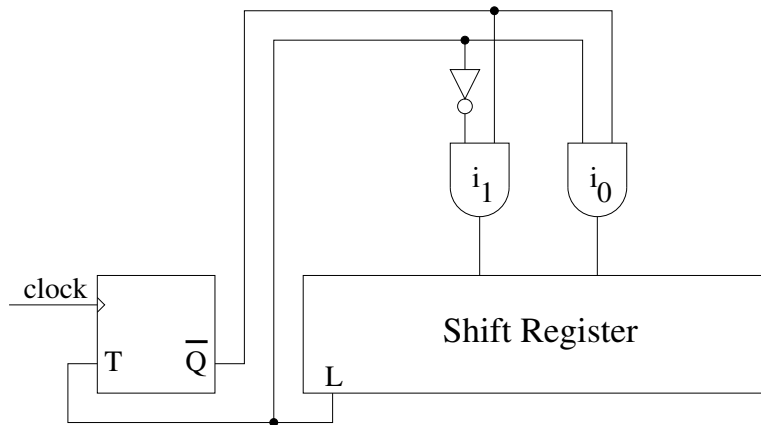

Problem 5.

(a)

 

(b)

v_2	v_1	v_0	x_1	x_0	v'_2	v'_1	v'_0	T_2	D_1	D_0	z_1	z_0
0	1	1	0	0	0	1	1	0	1	1	0	1
0	1	1	0	1	1	0	1	1	0	1	0	1
0	1	1	1	1	1	1	0	1	1	0	0	1
1	1	0	0	0	1	0	1	0	0	1	1	0
1	1	0	0	1	1	1	0	0	1	0	1	0
1	1	0	1	1	1	0	1	0	0	1	1	0
1	0	1	0	0	1	1	0	0	1	0	1	0
1	0	1	0	1	0	1	1	1	1	1	1	0
1	0	1	1	1	0	1	1	1	1	1	1	0

(c)

$$\begin{aligned}
 T_2 &= x_0 v_0 \\
 D_1 &= \overline{v_2} v_1 v_0 \overline{x_1} x_0 \vee v_2 v_1 \overline{v_0} \overline{x_1} \overline{x_0} \vee v_2 v_1 \overline{v_0} x_1 x_0 \\
 D_2 &= \overline{v_2} v_1 v_0 x_1 x_0 \vee v_2 v_1 \overline{v_0} \overline{x_1} x_0 \vee v_2 \overline{v_1} v_0 \overline{x_1} \overline{x_0} \\
 z_1 &= v_2 \\
 z_0 &= \overline{v_2} \quad (\text{or } z_0 = v_0 v_1)
 \end{aligned}$$