Adder

In order to construct a CPU, we need to perform arithmetic and logical operations. Basic arithmetic operator: addition

What's involved in adding binary numbers?

carry	0	1	1	0		decimal
		0	0	1	1	3
		0	1	1	0	6
	result	1	0	0	1	9

In each column:

input: add 2 bits, along with a carry bit from the previous result output: 1 bit result, 1 bit carry

Half-adder

adds 2 bits (x, y), generates sum (s) and carry (c) (note that previous carry is being ignored)

Truth table

_	x	У	ន	С			
-	0	0	0	0			
	0	1	1	0			
	1	0	1	0			
	1	1	0	1			

Boolean expressions:

 $s = \langle xy + x \rangle y = x XOR y$


$$c = xy$$


Half adder: circuit

$$s = \langle xy + x \rangle y = x XOR y$$

$$c = xy$$

Circuit:

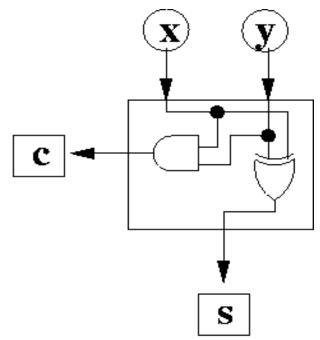

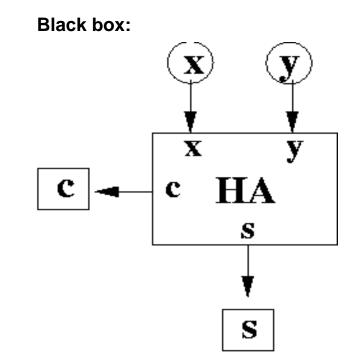

Full adder

In order to perform true addition, we need to use the carry from the previous result **Full adder**

```
Data inputs: x, y, c<sub>in</sub> (carry in)
Data outputs: s, c<sub>out</sub> (carry out)
```

Truth table

x	У	$\mathtt{c}_{\mathtt{in}}$	ន	$\mathtt{c}_{\mathtt{out}}$			
0	0	0	0	0			
0	0	1	1	0			
0	1	0	1	0			
0	1	1	0	1			
1	0	0	1	0			
1	0	1	0	1			
1	1	0	0	1			
1	1	1	1	1			

Boolean expressions

$$s = \langle x \rangle yc_{in} + \langle xy \rangle c_{in}$$
$$+ x \langle y \rangle c_{in} + xyc_{in}$$

$$c_{out} = \langle xyc_{in} + x \langle yc_{in} \rangle$$


+ $xy \langle c_{in} + xyc_{in} \rangle$

Ripple carry adder

adding k-bit values

ripple-carry adder: combine k 1-bit full adders

3-bit ripple-carry adder

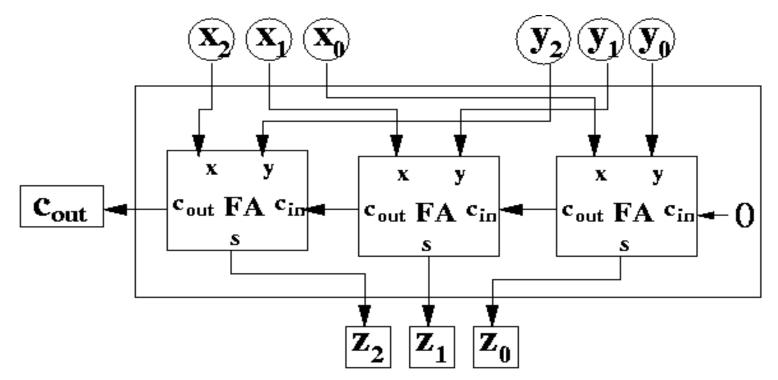

Notice that 0 is hard-wired as carry-in for rightmost full adder (could have used half adder)

Adder delay

Ripple-carry adder is logically correct, but may be slow. Each circuit requires a finite amount of time to give stable outputs when inputs change. Circuits are working in parallel, but it takes a finite amount of time before the carry-in from one circuit is available for the next one to use. Assume time T for each FA to generate output. n-bit ripple carry adder has O(n) delay: nT Speed can be improved by using "carry-lookahead": compute carries in parallel This document was created with Win2PDF available at http://www.daneprairie.com. The unregistered version of Win2PDF is for evaluation or non-commercial use only.