

Registers


Flip-flops are the basic building blocks for registers

Parallel-load register (32-bit) has 2 operations

c (control) = 0: hold


c (control) = 1: load ($z_{31-0} = x_{31-0}$)


Block diagram

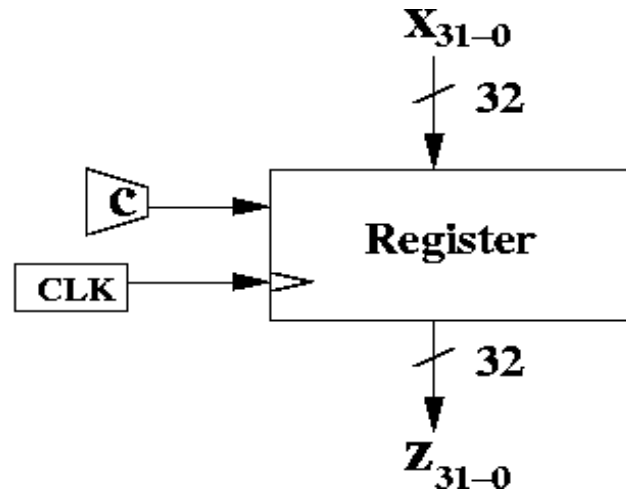

Don't forget the clock!

Example: 4 bits, using D flip-flops

 

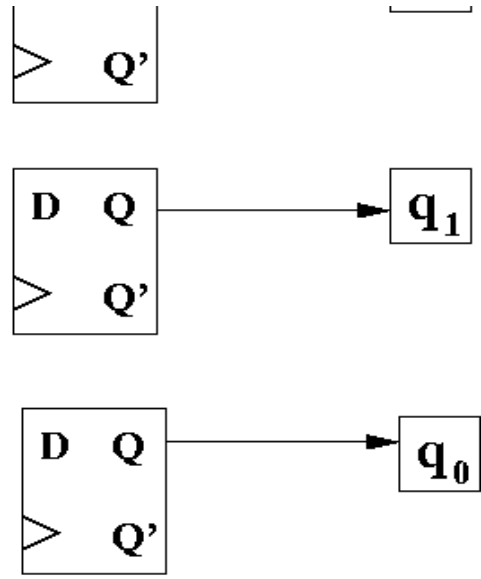

Registers

Need to choose inputs: hold or parallel load


Use 2-1 MUX

Hold: need to keep value constant

D flip-flop sets Q to value of D
feed Q back to 0 input of MUX

Parallel load: set flip-flop value to input
feed input x to 1 input of MUX

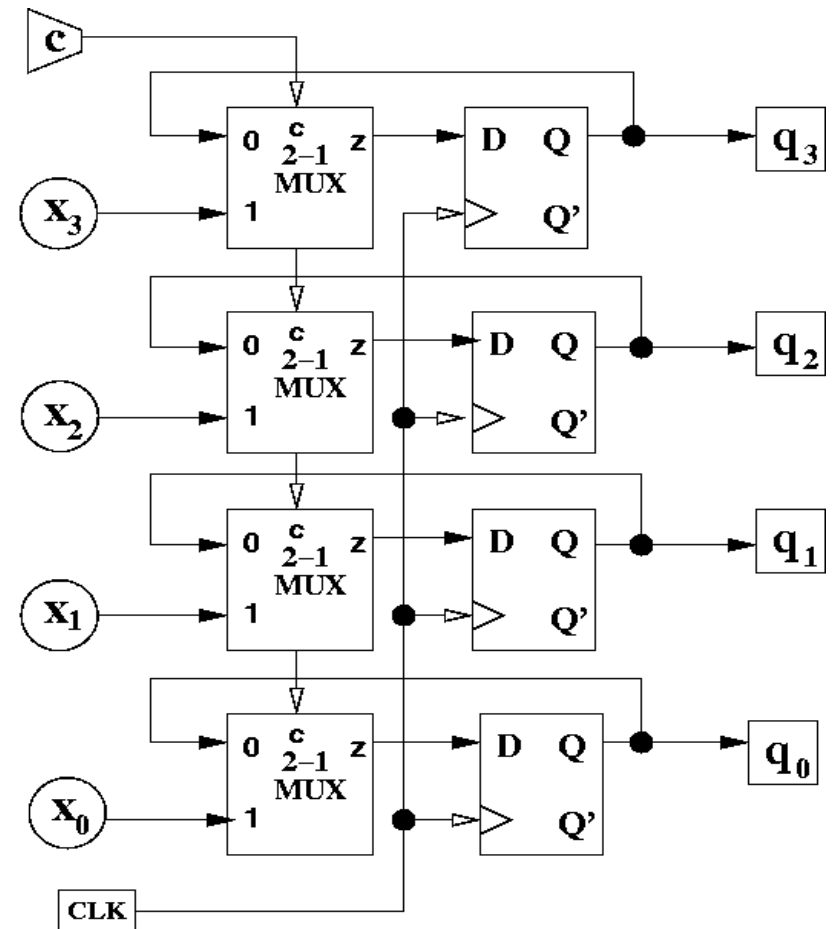Also need clock and control input
(Note that control is shown going
through each MUX)



Registers: T flip-flops

Register with T flip-flops: for simplicity, implement with 2 flip-flops

How does T flip-flop hold the value?

$$T = 0$$


How does it load?

$T = 1$ toggles

If $(x \neq Q)$, then toggle

MUX input 1:

$$T = x \text{ XOR } Q$$

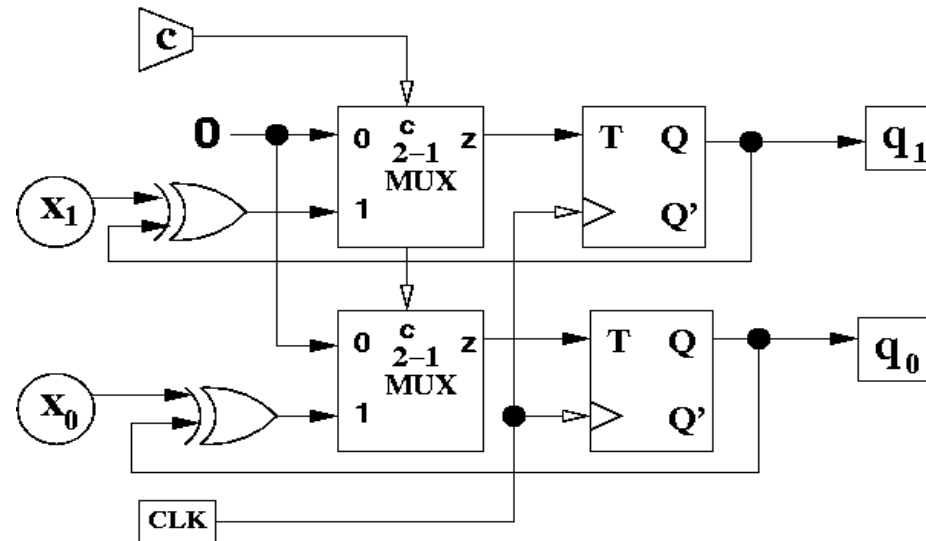

What other operations could we do?

Shift is simply another form of load!

Input is from current state, rather than external

Shift left: load bit i with value of bit $(i-1)$

Shift right: load bit i with value of bit $(i+1)$

Can add more control bits to select shift operations as well as regular load

Change MUX to 4-1:

control	operation
00	hold
01	parallel load
10	shift left logical 1 bit
11	shift right logical 1 bit

This document was created with Win2PDF available at <http://www.daneprairie.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.