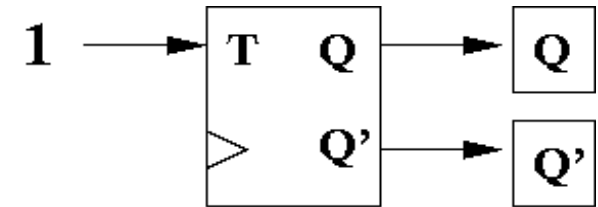



Counter

Counter increments an unsigned binary value from 0 to N

Consider a T flip-flop with hardwired input of 1:



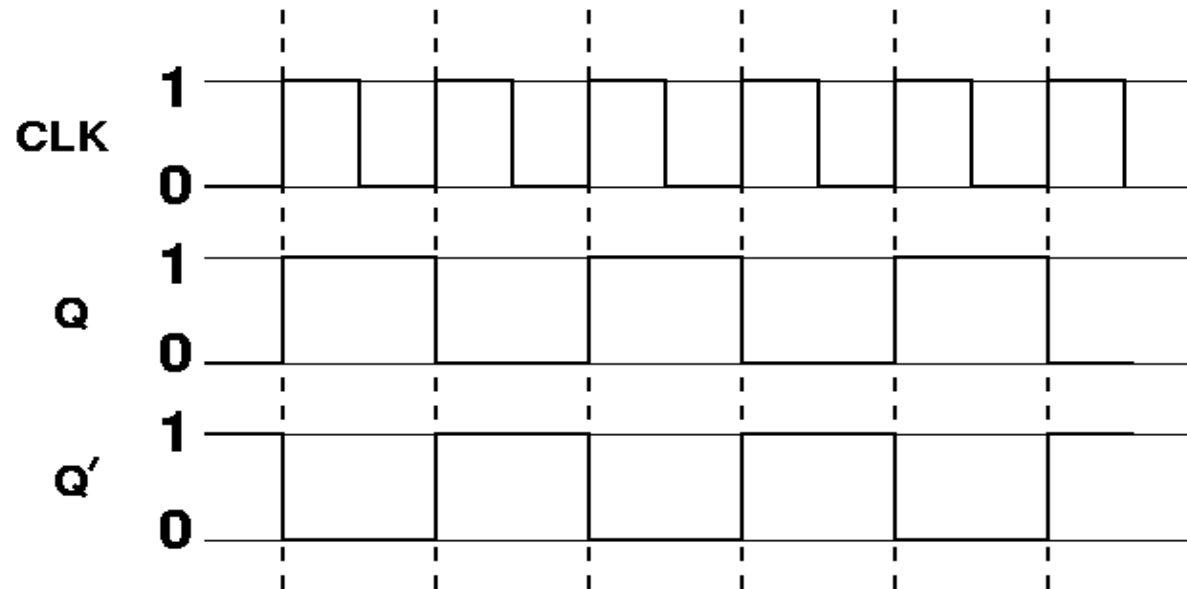The behavior can be represented by a timing diagram:




Value of Q toggles at each positive clock edge.

Notice that if the clock period is t , the period of the output Q

is exactly double the clock period, or $2t$.

Counter

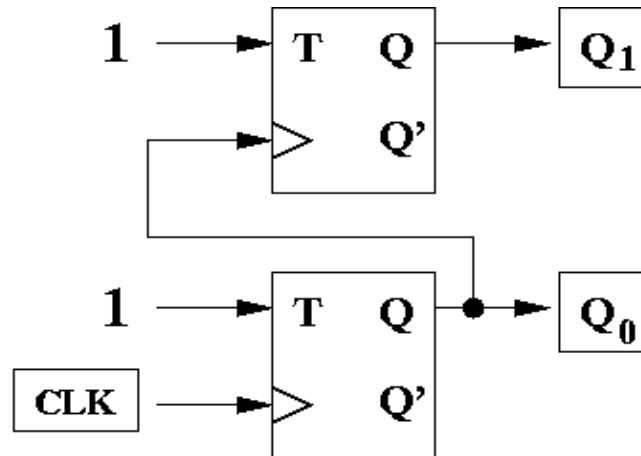Now use the output of the first flip-flop as the clock input of another T flip-flop:



What will be the period of the second flip-flop output Q₁?

If we keep repeating this N times, the period of the Nth output will be $2^N t$

How does this help build a counter?

Counter

Consider what it means to count in binary:

x_2	x_1	x_0	value
0	0	0	0
0	0	1	1
0	1	0	2
0	1	1	3
1	0	0	4
1	0	1	5
1	1	0	6
1	1	1	7

The sequence of x_0 values looks like a clock with period 1: 0 1 0 1 0 1 0 1

The sequence of x_1 values looks like a clock with period 2: 0 0 1 1 0 0 1 1

The sequence of x_2 values looks like a clock with period 4: 0 0 0 0 1 1 1 1

However, notice when x_1 changes relative to x_0 :

x_1 goes from 0 to 1 (for example, value 1 to 2) when x_0 goes from 1 to 0


x_1 goes from 1 to 0 (for example, value 3 to 4) when x_0 goes from 1 to 0

This means that we need to toggle x_1 when x_0 is on a negative edge,


but we want to use positive-edge flip-flops.

Counter

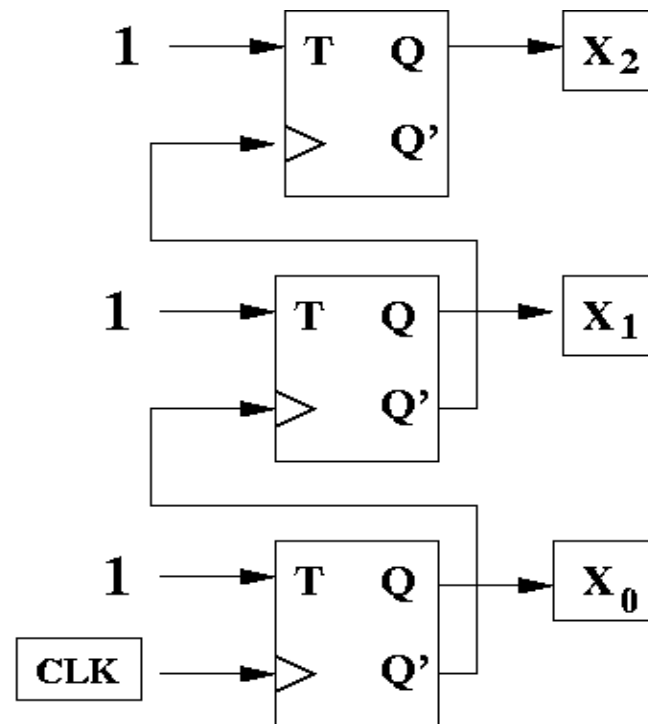Toggling Q_1 on a negative edge of Q_0 is the same as toggling Q_1 on a positive edge of Q_0' , so connect the negated output Q' of each flip-flop to the input of the next flip-flop:



Timing diagram for this 3-bit counter:

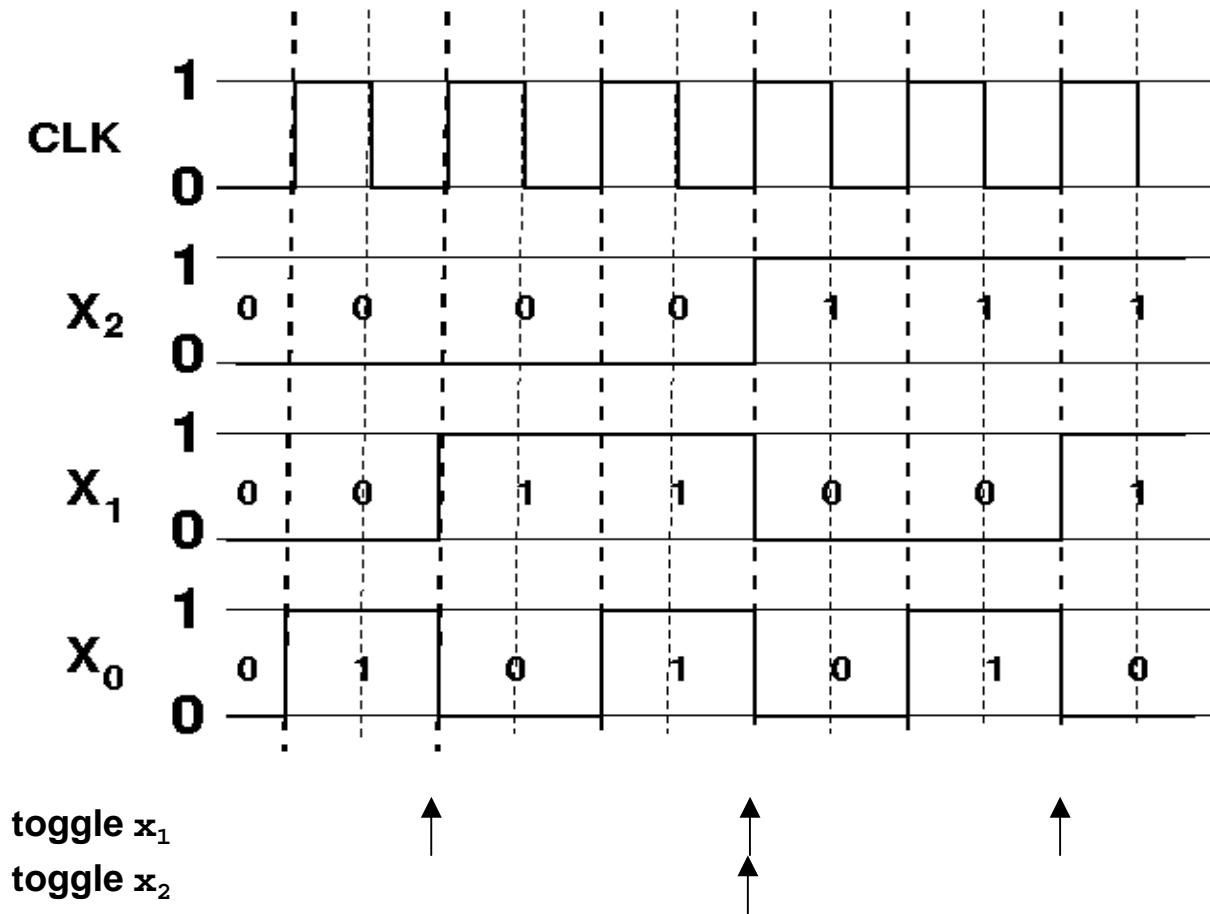

Read values in each column from left to right:

000, 001, 010, . . .

Variation: how would we use D flip-flops instead of T flip-flops?

This document was created with Win2PDF available at <http://www.daneprairie.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.