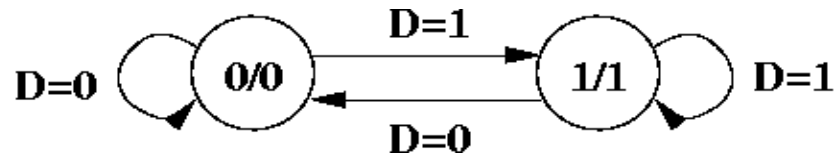


Finite state machines: flip-flop

Flip-flop can be modeled as a finite-state machine



D flip-flop

| | q | D | q^+ | z | T |
|-------------------------------|-----|-----|-------|-----|-----|
| State: 1 bit (q) | 0 | 0 | 0 | 0 | 0 |
| Input: 1 bit (D) | 0 | 1 | 1 | 0 | 1 |
| Output: current state (z) | 1 | 0 | 0 | 1 | 1 |
| | 1 | 1 | 1 | 1 | 0 |

In state 0:

input 0 gives new state 0 (reset)
input 1 gives new state 1 (set)


In state 1:

input 0 gives new state 0 (reset)
input 1 gives new state 1 (set)

Could implement this in the obvious way with a D flip-flop, or use a T flip-flop!

Finite state machines: flip-flop

T flip-flop:

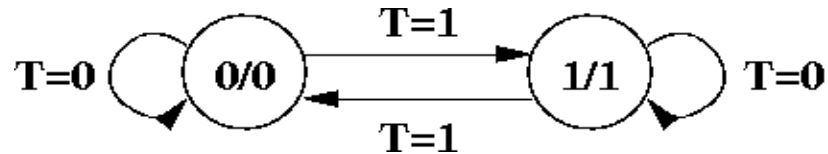

| | q | T | q^+ | z | D |
|-------------------------------|-----|-----|-------|-----|-----|
| State: 1 bit (q) | 0 | 0 | 0 | 0 | 0 |
| Input: 1 bit (T) | 0 | 1 | 1 | 0 | 1 |
| Output: current state (z) | 1 | 0 | 1 | 1 | 1 |
| | 1 | 1 | 0 | 1 | 0 |

In state 0:

input 0 gives new state 0 (hold)
input 1 gives new state 1 (toggle)


In state 1:

input 0 gives new state 1 (hold)
input 1 gives new state 0 (toggle)

Note that we can implement either type of flip-flop with the other type and some combinational circuit

Finite state machines: flip-flop

JK flip-flop:

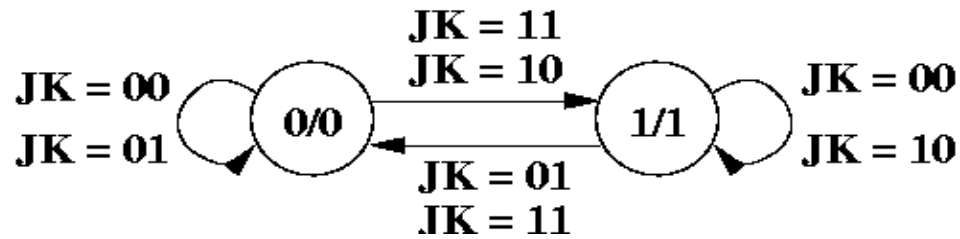

| | q | J | K | q^+ | z | |
|-------------------------------|-----|---|---|-------|---|--------|
| State: 1 bit (q) | 0 | 0 | 0 | 0 | 0 | hold |
| Input: 2 bits (JK) | 0 | 0 | 1 | 0 | 0 | reset |
| Output: current state (z) | 0 | 1 | 0 | 1 | 0 | set |
| | 0 | 1 | 1 | 1 | 0 | toggle |
| | 1 | 0 | 0 | 1 | 1 | hold |
| | 1 | 0 | 1 | 0 | 1 | reset |
| | 1 | 1 | 0 | 1 | 1 | set |
| | 1 | 1 | 1 | 0 | 1 | toggle |

Input is 2 bits, so there are 4 outgoing arcs from each state, but 2 pairs are equivalent

This can be implemented with either a T or D flip-flop

This document was created with Win2PDF available at <http://www.daneprairie.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.