

WARNING: THIS HW IS TWO PAGES LONG!!!!!!!!!!!!!!!!!!!!!!

1. (40 points)

- (a) (20 points) We are working in binary so all numbers are 0's and 1's. When we input 2 bits to a circuit we think of it as a NUMBER in base 2.

$$00=0$$

$$01=1$$

$$10=2$$

$$11=3$$

The output will be 3 bits, interpreted as a number in base 2.

$$000=0, \dots, 111=7$$

Write a truth table with 2 inputs and 3 outputs for the following function:

$$f(xy) = (xy)^2 \pmod{8}.$$

So for example

$f(11)$ is computed by $11=3$, $3^2 = 9$, $9 \pmod{8} = 1$, so the output is 001.

- (b) (20 points) Write a circuit for f using AND, OR, and NOT using the method shown in class (do not simplify- that would make it harder for the TA's to grade!)

SOLUTION TO PROBLEM 1 OMITTED

GO TO NEXT PAGE!!!!!!!!!!!!!!!!!!!!!!

2. (60 points) In this problem the inputs are considered bits that you add. So if the input is $(1, 0, 1)$ it is NOT 101 in base 2 which is 5. Its just three bits, separate.

The *Depth* of a circuit is the max number of gates from input to output.

The *Size* of a circuit is the total number of gates.

ALSO- we allow for input the variables AND their negations.

In this problem we will look at different circuits for:

$$f_n(x_1, \dots, x_n) = x_1 + \dots + x_n \pmod{2}.$$

We allow AND, OR and NOT gates usual; however, the AND and OR gates can take MANY inputs (as many as you want).

You can assume that n is a power of two if it makes the math easier.

- (a) (30 points) Show that, for all n , there is a circuit for f_n with depth 2. What is the circuit's size?
- (b) (30 points) Show that, for all n , there is a circuit for f_n with size $O(n)$ (less than some constant times n). What is the constant? What is the depth of the circuit? (HINT: First get a circuit for $f_2(x_1, x_2)$. View this as a gate you can use. Use that

$$f_n(x_1, \dots, x_n) = f_{n/2}(f_2(x_1, x_2), f(x_3, x_4), \dots, f(x_{n-1}, x_n)).$$

- (c) (0 points but think about) In part 1 you got a CONSTANT DEPTH but LARGE SIZE circuit. In part 2 you got a SMALL SIZE but LOG DEPTH circuit. Is there a circuit for f_n which is constant depth and small size?

SOLUTION TO PROBLEM 2

Omitted. Will go over in class.