

## Carry lookahead

Can calculate carries in parallel

Tradeoff: need more hardware (space vs. time)

Boolean expression for carry-out:

$$c_{out} = \overline{xy}c_{in} + x\overline{y}c_{in} + xy\overline{c_{in}} + xyzc_{in}$$

What does this expression look like?

$$z = \overline{abc} + a\overline{bc} + ab\overline{c} + abc$$

How many inputs? 3

How many need to be true? 2

What is that function called?

Alternate expression for carry-out:

$$c_{out} = xy + xc_{in} + yc_{in}$$

This means that there is a carry whenever at least 2 of the bits are 1 (possibly all 3).

Call  $c_{in}$   $c_i$  (carry-in for bit i) and  $c_{out}$   $c_{i+1}$  (carry-in for bit i+1)

Distributive property:

$$c_{i+1} = x_i y_i + c_i (x_i + y_i)$$

Define 2 new terms:

$$g_i = x_i y_i$$

$$p_i = x_i + y_i$$

Then rewrite expression for  $c_{i+1}$

$$c_{i+1} = g_i + p_i c_i$$

$g_i$  is called the **generate** term

it always generates a carry out, if equal to 1

$p_i$  is called the **propagate** term.

it may generate a carry, depending on the carry-in ( $c_i$ )

if exactly one of  $x_i$  or  $y_i$  is 1, then the carry-in will determine the carry-out

How can we get rid of the dependency on the carry-in?

Let's look at the first carry:

$$c_1 = g_0 + p_0 c_0$$

The next one is:

$$c_2 = g_1 + p_1 c_1$$

Now we can plug in the expression for  $c_1$ , which we just calculated:

$$\begin{aligned} c_2 &= g_1 + p_1 (g_0 + p_0 c_0) \\ &= g_1 + p_1 g_0 + p_1 p_0 c_0 \end{aligned}$$

How do we get the right side of this expression?

Since  $g_1$  and  $p_1$  depend only on  $x_1$  and  $y_1$ ,

and  $g_0$  and  $p_0$  depend only on  $x_0$  and  $y_0$ ,

and  $c_0$  depends only on  $x_0$  and  $y_0$  (there is no carry-in for the addition of bits 0),

we can get  $c_2$  right away without waiting for  $c_1$ !

Likewise,

$$\begin{aligned} c_3 &= g_2 + p_2 c_2 \\ &= g_2 + p_2 (g_1 + p_1 g_0 + p_1 p_0 c_0) \\ &= g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0 \end{aligned}$$


Following the same pattern,

$$C_4 = g_3 + p_3g_2 + p_3p_2g_1 + p_3p_2p_1g_0 + p_3p_2p_1p_0C_0$$

**The circuit uses full adders, but the output of one  
is not directly connected to the input of the next**

## Carry lookahead


Approximate circuit for 3 bits:

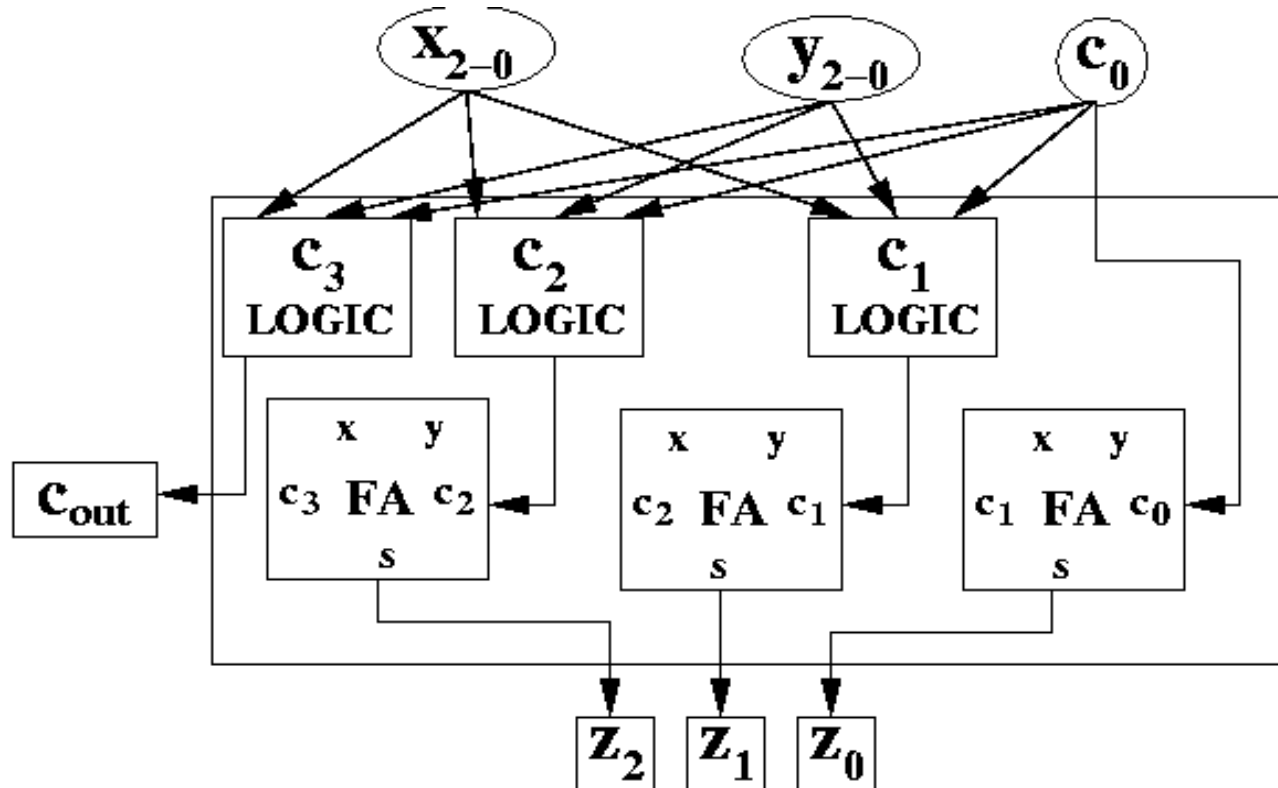

What's missing?

Need to show connections from  $x_i$  and  $y_i$  to the appropriate adders.

## Carry lookahead: circuit

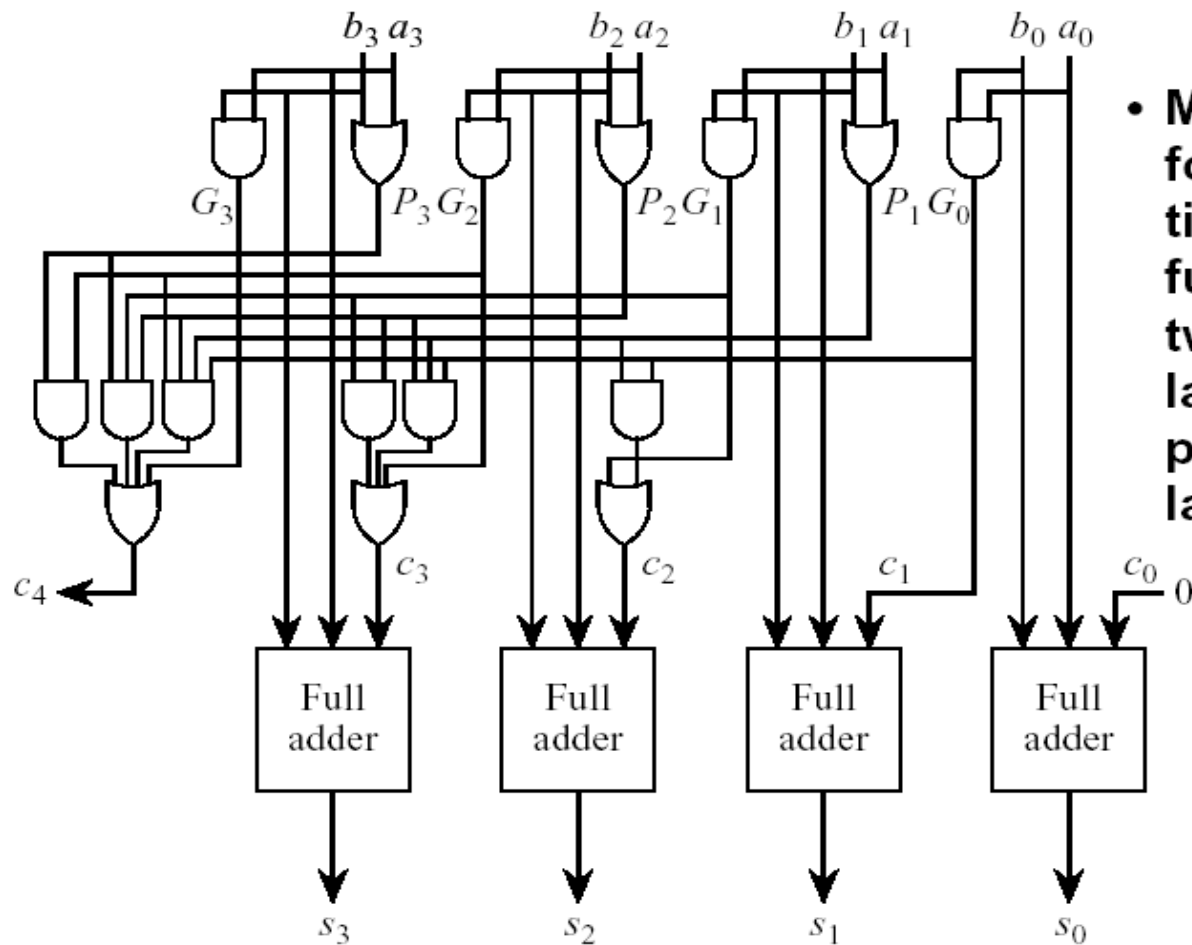

- Maximum gate delay for the carry generation is only 3. The full adders introduce two more gate delays. Worst case path is 5 gate delays.

## Carry lookahead: group

How much have we reduced the delay?

We would like to have  $O(1)$  time, but

note that there are  $i$  OR operations for the  $i$ th carry  $c_i$ ,  
and there are also  $i$  AND operations for the biggest term

There is a practical limit to the number of inputs to a single gate (fan-in).

We could build everything out of 2-input AND gates and OR gates, and the delay would be only  $O(\lg n)$  for  $n$  bits, which is still much better than  $O(n)$ .

Another approach:

Build 4-bit carry-lookahead units, then cascade them together in group of 4 to get 16-bit adder.

This can be done with a maximum fan-in of only 4.

This is called **group carry-lookahead** (GCLA)

Need to deal with propagates and generates between 4-bit blocks.

"Super" propagate:

A propagate will occur from one group of 4 to the next  
if every propagate in the first group is true.

$$P_0 = p_3 * p_2 * p_1 * p_0$$

Similarly:

$$P_1 = p_7 * p_6 * p_5 * p_4$$

$$P_2 = p_{11} * p_{10} * p_9 * p_8$$

$$P_3 = P_{15} * P_{14} * P_{13} * P_{12}$$

**"Super" generate:**

**A generate will occur between 4-bit groups**

**if there is a carry out from the most significant bit in the 4-bit group.**

**This occurs when:**

**Generate occurs for the most significant bit OR**

**Generate occurs for a lower bit and all intermediate propagates are true**

$$G_0 = g_3 + (p_3 * g_2) + (p_3 * p_2 * g_1) + (p_3 * p_2 * p_1 * g_0)$$

$$G_1 = g_7 + (p_7 * g_6) + (p_7 * p_6 * g_5) + (p_7 * p_6 * p_5 * g_4)$$

$$G_2 = g_{11} + (p_{11} * g_{10}) + (p_{11} * p_{10} * g_9) + (p_{11} * p_{10} * p_9 * g_8)$$

$$G_3 = g_{15} + (p_{15} * g_{14}) + (p_{15} * p_{14} * g_{13}) + (p_{15} * p_{14} * p_{13} * g_{12})$$

**Carry out:**

**Carry out for the 4-bit group is similar to the carry out for each bit:**


$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

$$C_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$$

## Carry lookahead: group

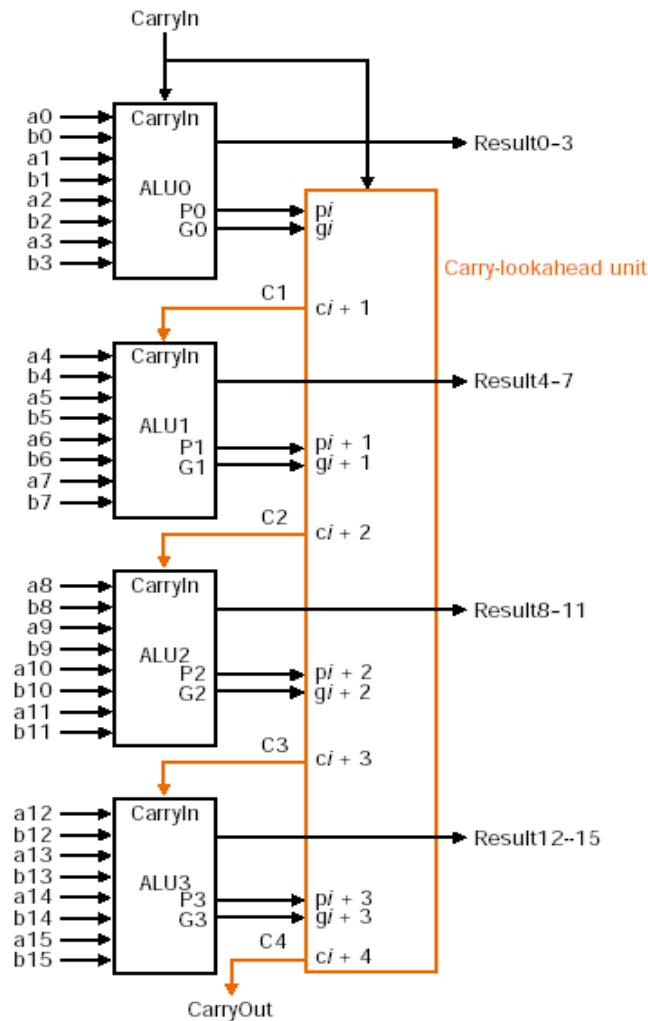

16-bit adder using carry-lookahead with 4-bit adders (Fig. 4.24)

Note that carry-in for each 4-bit adder is generated by carry-lookahead unit, not individual adders



## Carry-select

Another solution: carry-select adder

Design trick: When all else fails, **GUESS!** (precompute)

To build 8-bit adder:


Lower 4 bits: any adder (ripple-carry, carry-lookahead)

Upper 4 bits: 2 adders

First adder has carry-in of 1

Second adder has carry-in of 0

 Select between 2 upper results based on carry-out from lower result



2/10/03

©UCB Spring 2003

CS152 / Kubitowicz  
Lec4.35

Reference:

<http://www-inst.eecs.berkeley.edu/~cs152/>

Time required:

4-bit add time

Multiplexor to select

## Adder complexity

	Time	Space
Ripple-carry (RCA)	$O(n)$	$O(n)$
Carry-lookahead (CLA)	$O(\log n)$	$O(n \log n)$
Carry-select (CSA)	$O(\sqrt{n})$	$O(n)$

This document was created with Win2PDF available at <http://www.daneprairie.com>.  
The unregistered version of Win2PDF is for evaluation or non-commercial use only.