

START

RECORDING

# Circuits

CMSC250

# Circuits

- We can build circuits for addition, multiplication, division, bit shifting...
- Every logical operation we have learned ( $\sim, \wedge, \vee$ ) maps straightforwardly to a tiny piece of hardware called a *logical gate*.
- These gates connect to each other to make arbitrarily complicated circuits!

# From a truth table to a formula

<b>p</b>	<b>q</b>	<b>r</b>	<b>output</b>
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

# From a truth table to a formula

<b>p</b>	<b>q</b>	<b>r</b>	<b>output</b>
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

- Let us focus entirely on the rows that output 1!

p	q	r	output
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Focusing on the 1<sup>st</sup> row...

<b>p</b>	<b>q</b>	<b>r</b>	<b>output</b>
0	0	0	1

- Write a formula that is '1' only on inputs  $p = 0$ ,  $q = 0$ ,  $r = 0$ .

p	q	r	output
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Focusing on the 1<sup>st</sup> row...

p	q	r	output
0	0	0	1

- Write a simple formula that is '1' only on inputs p = 0, q = 0, r = 0.

$$\sim p \wedge \sim q \wedge \sim r$$

p	q	r	output
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Focusing on the 4<sup>th</sup> row...

<b>p</b>	<b>q</b>	<b>r</b>	<b>output</b>
0	1	1	1

- Same deal



p	q	r	output
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Focusing on the 4<sup>th</sup> row...

<b>p</b>	<b>q</b>	<b>r</b>	<b>output</b>
0	1	1	1

- Same deal

$$\sim p \wedge q \wedge r$$

p	q	r	output
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Focusing on the 5<sup>th</sup> row...

<b>p</b>	<b>q</b>	<b>r</b>	<b>output</b>
1	0	0	1

$$p \wedge \sim q \wedge \sim r$$

p	q	r	output
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Focusing on the 8<sup>th</sup> row...

<b>p</b>	<b>q</b>	<b>r</b>	<b>output</b>
1	1	1	1

$$p \wedge q \wedge r$$

How do we combine those simple formulae?

$$\sim p \wedge \sim q \wedge \sim r$$

$$\sim p \wedge q \wedge r$$

$$p \wedge \sim q \wedge \sim r$$

$$p \wedge q \wedge r$$

# How do we combine those simple formulae?

$$(\sim p \wedge \sim q \wedge \sim r) \vee$$

$$(\sim p \wedge q \wedge r) \vee$$

$$(p \wedge \sim q \wedge \sim r) \vee$$

$$(p \wedge q \wedge r)$$

p	q	r	output
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

- Outputs 1 if and only if the truth table outputs 1!

# How do we combine those simple formulae?

$$(\sim p \wedge \sim q \wedge \sim r) \vee$$

$$(\sim p \wedge q \wedge r) \vee$$

$$(p \wedge \sim q \wedge \sim r) \vee$$

$$(p \wedge q \wedge r)$$

p	q	r	output
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

- Outputs 1 if and only if the truth table outputs 1!
- **We want to do this in hardware!**


# Logical gates

- The smallest pieces of hardware that we will examine are called ***logical gates***.
- Most gates for this course will take **bits** as inputs and will emit one **bit** as output. (Not all gates have this property)



- Those gates can connect to each other in various different ways in order to create more complex circuits

# Our first gate

 

<i>A</i>	<i>out</i>
0	1
1	0

- This gate is known as the **inverter**.
- It corresponds **exactly** to the negation operation in propositional logic!
  - Where 1, set True.
  - Where 0, set False



# Our second gate



$p$	$q$	$r$
0	0	0
0	1	0
1	0	0
1	1	1

- Corresponds to:

Conjunction


Disjunction

# Our second gate (AND gate)




$p$	$q$	$r$
0	0	0
0	1	0
1	0	0
1	1	1

- Corresponds to:

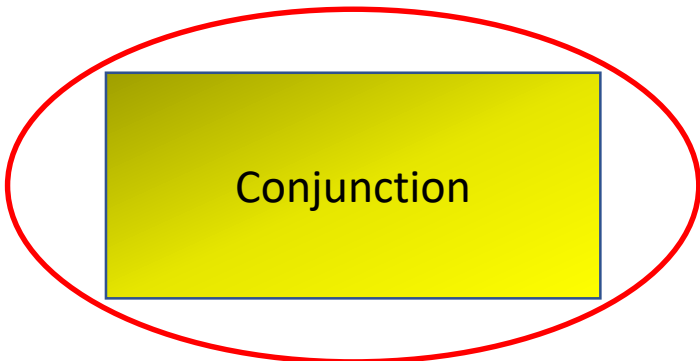

# Our second gate (AND gate)

 

$p$	$q$	$r$
0	0	0
0	1	0
1	0	0
1	1	1

- Corresponds to:

Conjunction

Disjunction

# Our third gate (OR gate)



$p$	$q$	$r$
0	0	0
0	1	1
1	0	1
1	1	1

- Corresponds to logical disjunction (OR)

# Our fourth and fifth gate (NAND and NOR gate)




$p$	$q$	$r$
0	0	1
0	1	1
1	0	1
1	1	0



$p$	$q$	$r$
0	0	1
0	1	0
1	0	0
1	1	0

 
# Exercises

- Which boolean function does this circuit correspond to?


 
# Exercises


- Which boolean function does this circuit correspond to?



$$(p \wedge s) \vee r$$

# Exercises


- And this?

 




# Exercises

- And this?

 


$$(m \wedge n) \vee (\sim (k \wedge l))$$

And this?

 


And this?

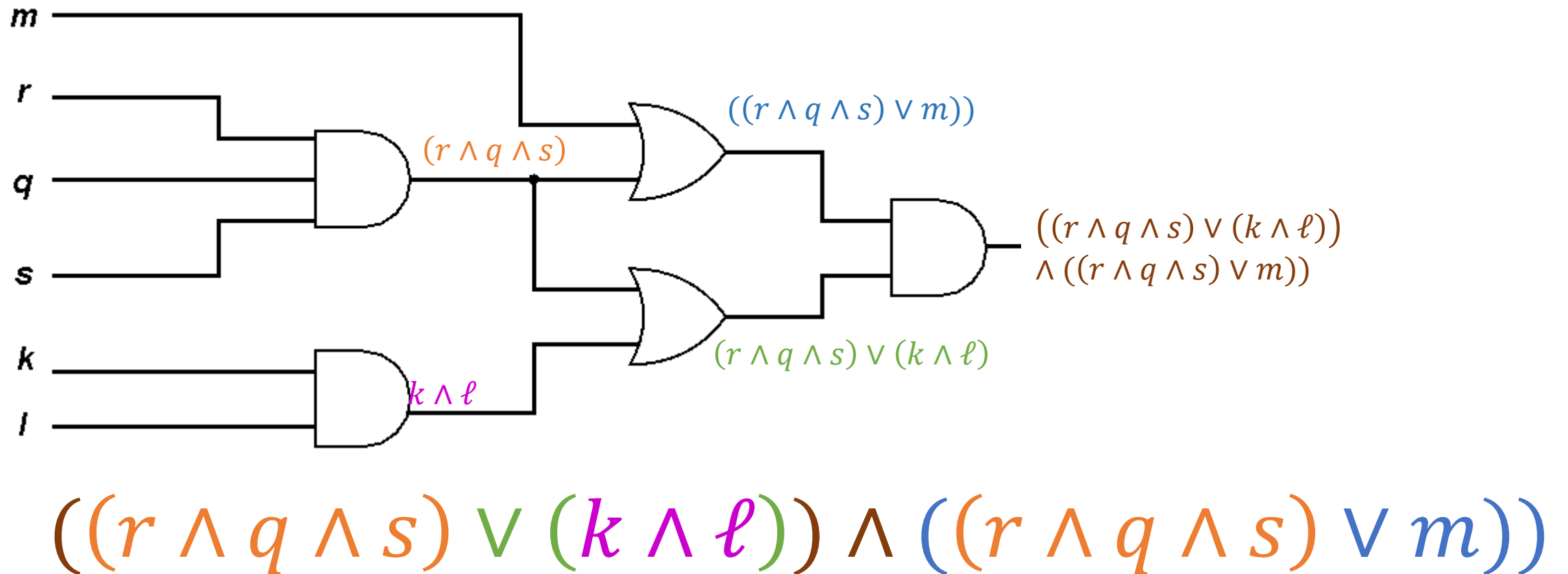

And this?


Can we make this circuit *cheaper*?

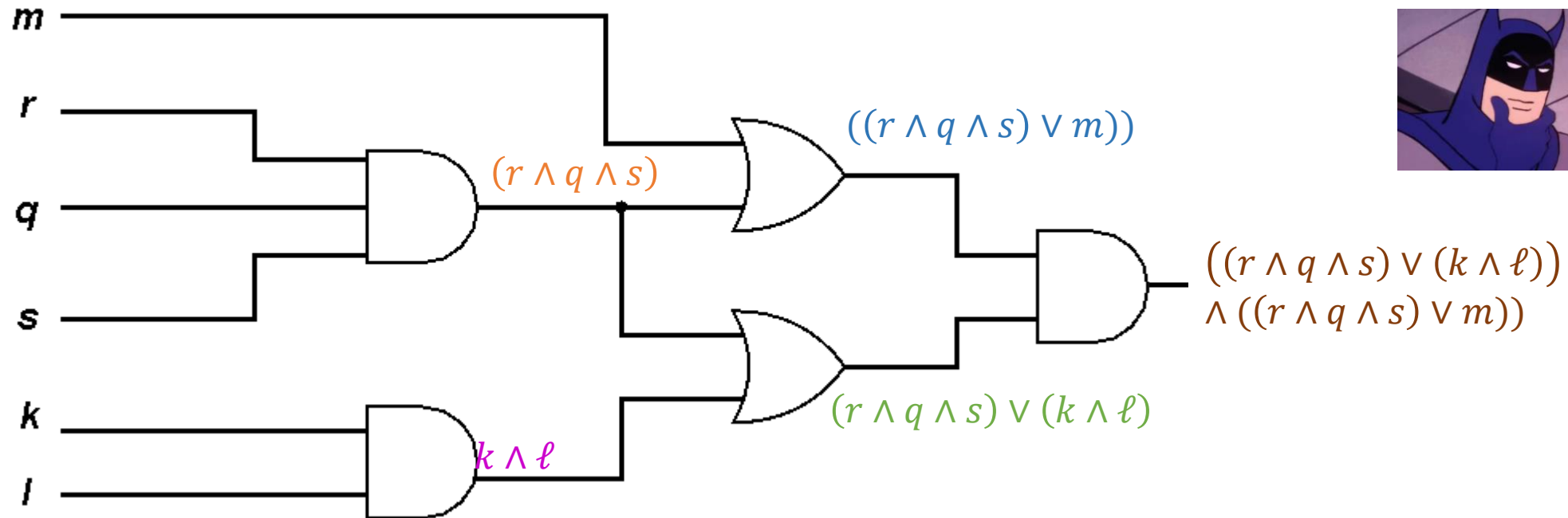


$$((r \wedge q \wedge s) \vee (k \wedge \ell)) \wedge ((r \wedge q \wedge s) \vee m)$$
 
# Simplifying the circuit...

$$\begin{aligned} & ((r \wedge q \wedge s) \vee (k \wedge \ell)) \wedge ((r \wedge q \wedge s) \vee m) \\ \equiv & (r \wedge q \wedge s) \vee ((k \wedge \ell) \wedge m) \end{aligned}$$




**New circuit: Three gates**

 

**Old circuit: Five gates**


# Exercises

 1. Which logical expression is computed by the following circuit?



# Exercises

 1. Which logical expression is computed by the following circuit?
2. *Simplify* the circuit as much as possible!



Coming back to our original formula...

$$(\sim p \wedge \sim q \wedge \sim r) \vee (\sim p \wedge q \wedge r) \vee (p \wedge \sim q \wedge \sim r) \vee (p \wedge q \wedge r)$$



Coming back to our original formula...


$$(\sim p \wedge \sim q \wedge \sim r) \vee (\sim p \wedge q \wedge r) \vee (p \wedge \sim q \wedge \sim r) \vee (p \wedge q \wedge r)$$

- For each small formula we have a circuit, and we will combine with a 4-input OR gate!

Coming back to our original formula...


$$(\sim p \wedge \sim q \wedge \sim r) \vee (\sim p \wedge q \wedge r) \vee (p \wedge \sim q \wedge \sim r) \vee (p \wedge q \wedge r)$$

 - For each small formula we have a circuit, and we will combine with a 4-input OR gate!




# Circuit 1

$$(\sim p \wedge \sim q \wedge \sim r)$$

 


# Circuit 2

$$(\sim p \wedge q \wedge r)$$

 


# Circuit 3

$$(p \wedge \sim q \wedge \sim r)$$

 

# Circuit 4

$$(p \wedge q \wedge r)$$

 


# Building Adder Circuits

- We want to build circuits that add arbitrarily large binary numbers.
- E.g

$$\begin{array}{r} 10011001 \\ +00110011 \\ \hline 11001100 \end{array}$$

Inputs

Output

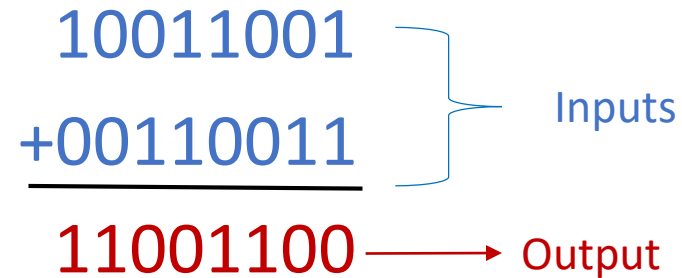

# Half-Adder

- A half-adder is a circuit that adds **two bits** together!

$$\begin{array}{r} X \\ + Y \\ \hline C S \end{array}$$

- (Remember:  $C$  is the carry bit.)
- Let's try to build a circuit that computes both  $S$  and  $C$ !



# Truth table


<b>X</b>	<b>Y</b>	<b>S</b>	<b>C</b>
0	0	?	?
0	1	?	?
1	0	?	?
1	1	?	?

# Truth table

<b>X</b>	<b>Y</b>	<b>S</b>	<b>C</b>
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


# Truth table

X	Y	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

# Truth table

X	Y	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

# Making XOR cheaper


- First, let's convince ourselves that

$$(x \oplus y) \equiv (x \wedge (\sim y)) \vee ((\sim x) \wedge y) \equiv (x \vee y) \wedge (\sim(x \wedge y))$$
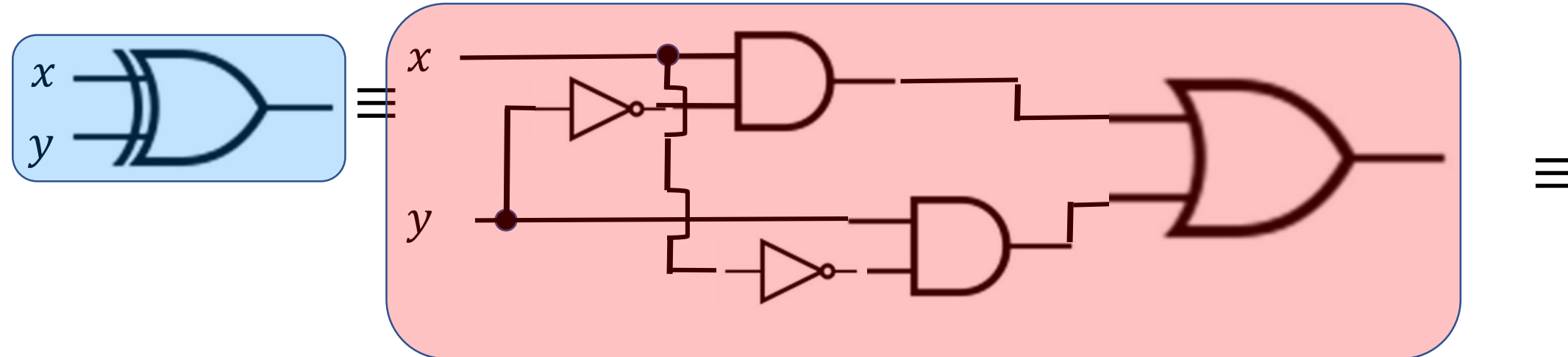
# Making XOR cheaper

- First, let's convince ourselves that


$$(x \oplus y) \equiv (x \wedge (\sim y)) \vee ((\sim x) \wedge y) \equiv (x \vee y) \wedge (\sim(x \wedge y))$$


 
# Making XOR cheaper

- First, let's convince ourselves that


$$(x \oplus y) \equiv (x \wedge (\sim y)) \vee ((\sim x) \wedge y) \equiv (x \vee y) \wedge (\sim(x \wedge y))$$


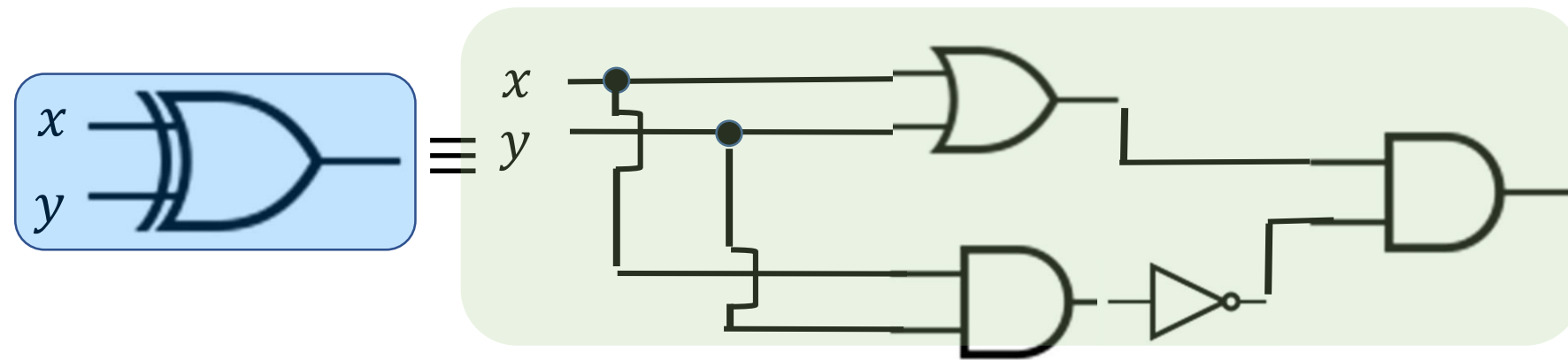
# Making XOR cheaper

- First, let's convince ourselves that

$$(x \oplus y) \equiv (x \wedge (\sim y)) \vee ((\sim x) \wedge y) \equiv (x \vee y) \wedge (\sim(x \wedge y))$$




From **five** gates to **four**!





 
# Optimizing Half Adder

- We can now **optimize** the Half Adder.
- We won't just use simplified XOR, but also **leverage simplified XOR** to **re-use** the **AND** gate used to compute the carry bit  $C$ !



# Half Adder Abstraction

 

4 gates, instead of 6 for the previous one!

# Half Adder Abstraction



# Full-Adder

- Now, let's consider the complete case, where we want to build a circuit that computes the sum of two 2-digit binary numbers:

$$\begin{array}{r} P Q \\ + \underline{W X} \\ C S_1 S_2 \end{array}$$

- To do this, we also need the ability to add 3 digits, because:

$$\begin{array}{r} \underline{C_1} \\ P Q \\ + \underline{W X} \\ C S_1 S_2 \end{array}$$

# Full-Adder

- Now, let's consider the complete case, where we want to build a circuit that computes the sum of two 2-digit binary numbers:

$$\begin{array}{r} P Q \\ + \underline{W X} \\ C S_1 S_2 \end{array}$$

- To do this, we also need the ability to add 3 digits, because:

$$\begin{array}{r} \underline{C_1} \\ P Q \\ + \underline{W X} \\ C S_1 S_2 \end{array}$$

*We will call a circuit that adds 3 bits a full adder*

We could do the truth table....

P Q  
+ W X  
C S1 S2

P	Q	W	X	C	S <sub>1</sub>	S <sub>2</sub>
0	0	0	0			
0	0	0	1			
0	0	1	0			
0	0	1	1			
0	1	0	0			
0	1	0	1			
0	1	1	0			
0	1	1	1			
1	0	0	0			
1	0	0	1			
1	0	1	0			
1	0	1	1			
1	1	0	0			
1	1	0	1			
1	1	1	0			
1	1	1	1			

We could do the truth table....

P Q  
+ W X  
C S1 S2

P	Q	W	X	C	S <sub>1</sub>	S <sub>2</sub>
0	0	0	0			
0	0	0	1			
0	0	1	0			
0	0	1	1			
0	1	0	0			
0	1	0	1			
0	1	1	0			
0	1	1	1			
1	0	0	0			
1	0	0	1			
1	0	1	0			
1	0	1	1			
1	1	0	0			
1	1	0	1			
1	1	1	0			
1	1	1	1			

But it's time  
consuming and we  
are all busy people

# Constructing a Full-Adder in another way


- We need to build a circuit that computes the sum of 3 digits, e.g  $P + Q + R$

- **Step 1:** Compute 
$$\begin{array}{r} P \\ + Q \\ \hline C_1 S_1 \end{array}$$
 with a **half-adder**:







# Constructing a Full Adder

 

 - Step 2: Compute  $\begin{array}{r} + \\ \underline{R} \\ C_2S \end{array}$  with another half-adder:




# Constructing a full-adder

 


- **Step 3:** Combine  $C_1$  and  $C_2$  with an OR gate to yield the final carry bit  $C$ .

# Constructing a full-adder

 

- **Step 3:** Combine  $C_1$  and  $C_2$  with an OR gate to yield the final carry bit  $C$ .
- Why did we choose an OR gate to combine the “intermediate” carries  $C_1$  and  $C_2$ ?

# Constructing a full-adder

 

- **Step 3:** Combine  $C_1$  and  $C_2$  with an OR gate to yield the final carry bit  $C$ .

**Abstraction  
time!**

# Full Adder Black Box

- 3 inputs, 2 outputs




# 2-bit adder

- However, **we still have not solved our original problem**, which is to construct a circuit that adds 2-bit numbers!


$$\begin{array}{r} P\ Q \\ + \underline{W\ X} \\ C\ S_1\ S_2 \end{array}$$

 - So, we need a circuit that takes 4 inputs and emits 3 outputs:



 
# Constructing a 2-bit adder

- Step 1: Take care of the **right-most column** with a **half-adder**:


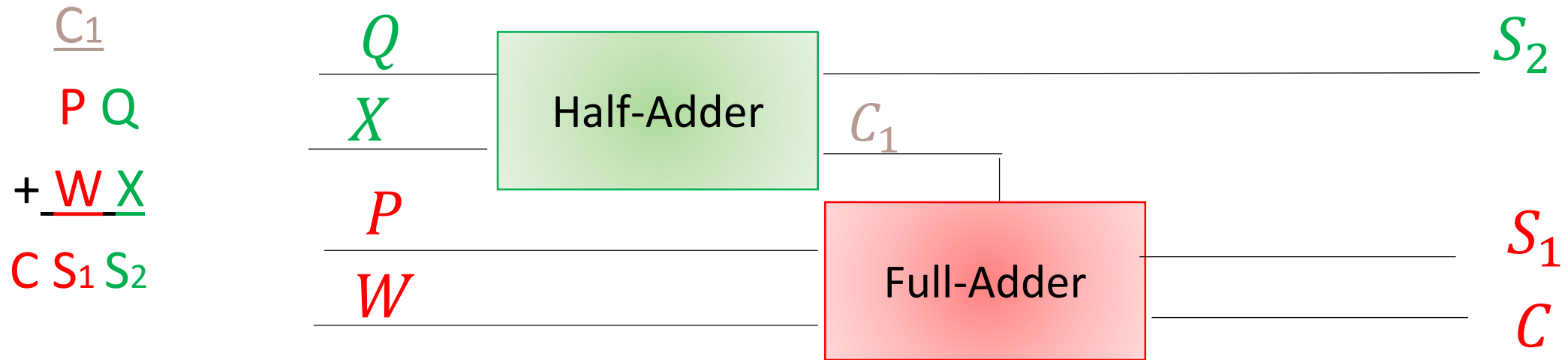
# Constructing a 2-bit adder

- Step 1: Take care of the **right-most column** with a **half-adder**:




- Step 2 (and final): Connect **Half-Adder** and new inputs to **Full-adder** appropriately to produce final circuit.


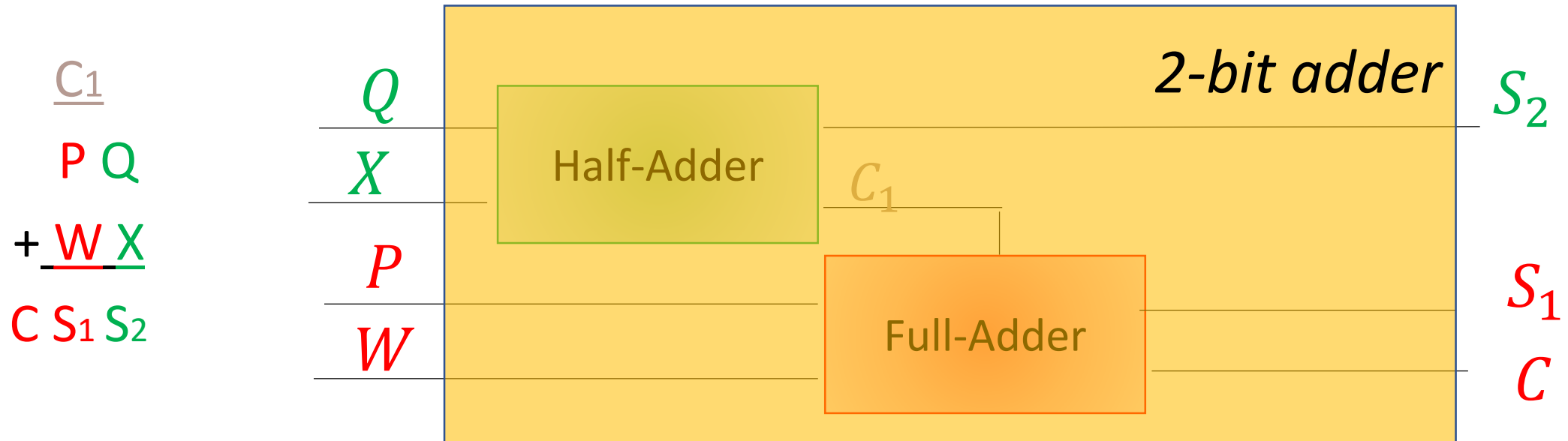
# Constructing a 2-bit adder


- Step 1: Take care of the **right-most column** with a **half-adder**:





- Step 2 (and final): Connect **Half-Adder** and new inputs to **Full-adder** appropriately to produce **final circuit**.
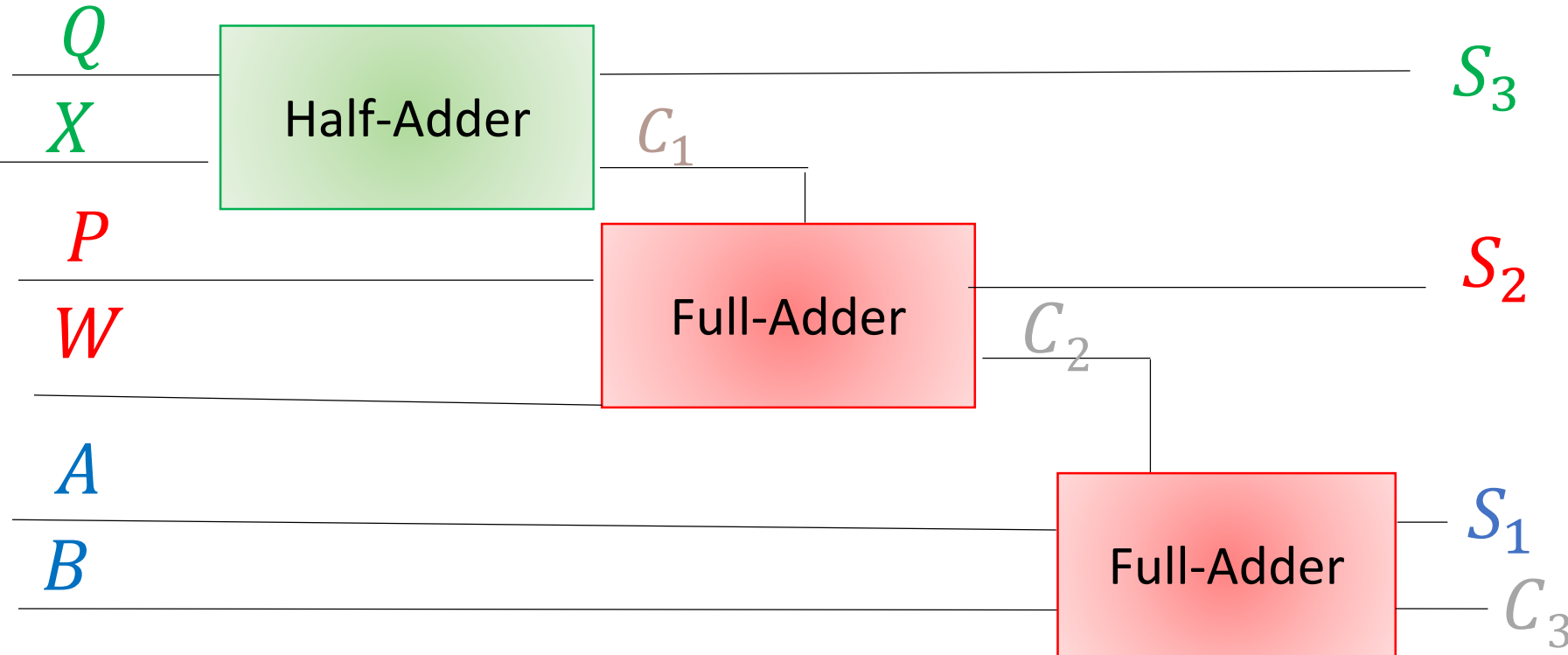
# Constructing a 3-bit adder (messy)


$$\begin{array}{r} \phantom{+} \underline{C_2} \underline{C_1} \\ \phantom{+} A \ P \ Q \\ + \underline{B} \ \underline{W} \ \underline{X} \\ \hline C_3 \ S_1 \ S_2 \ S_3 \end{array}$$




# Constructing a 3-bit adder (neat)

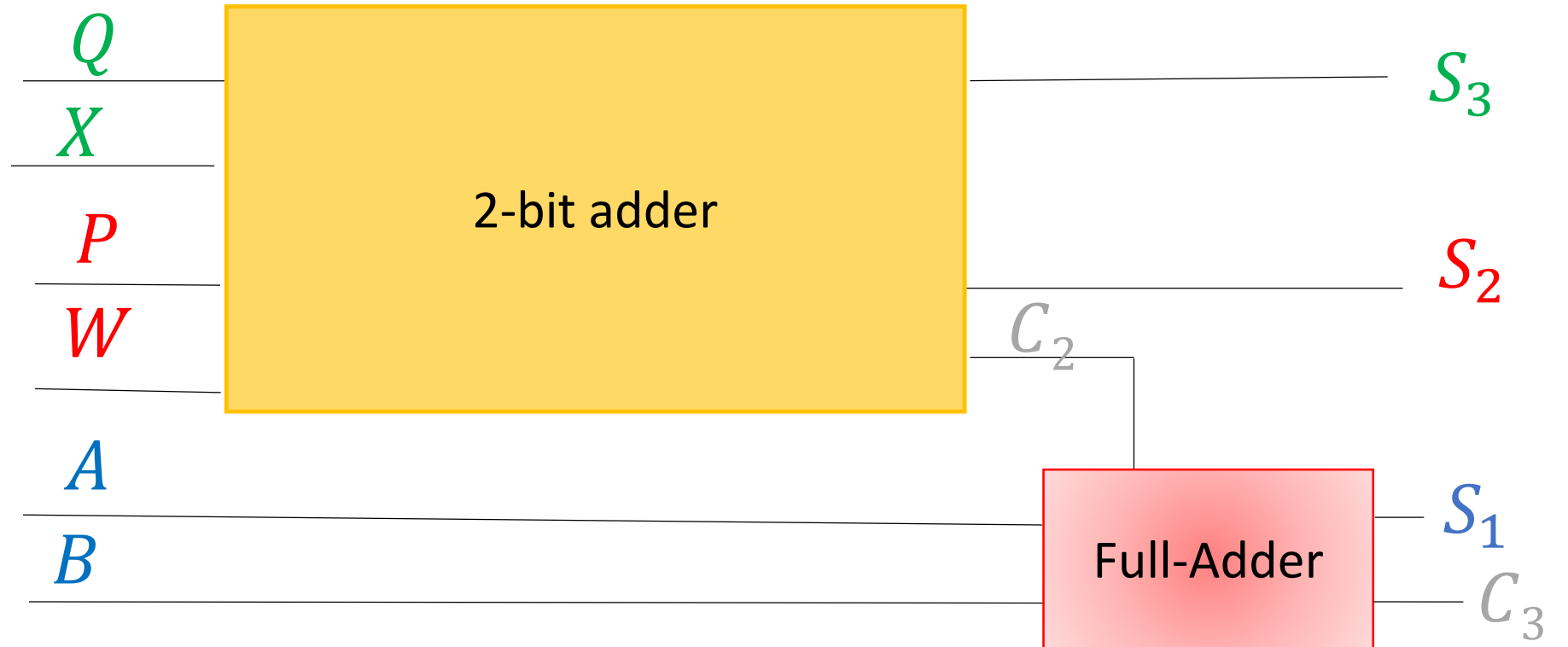 

# Constructing an n-bit adder (messy)

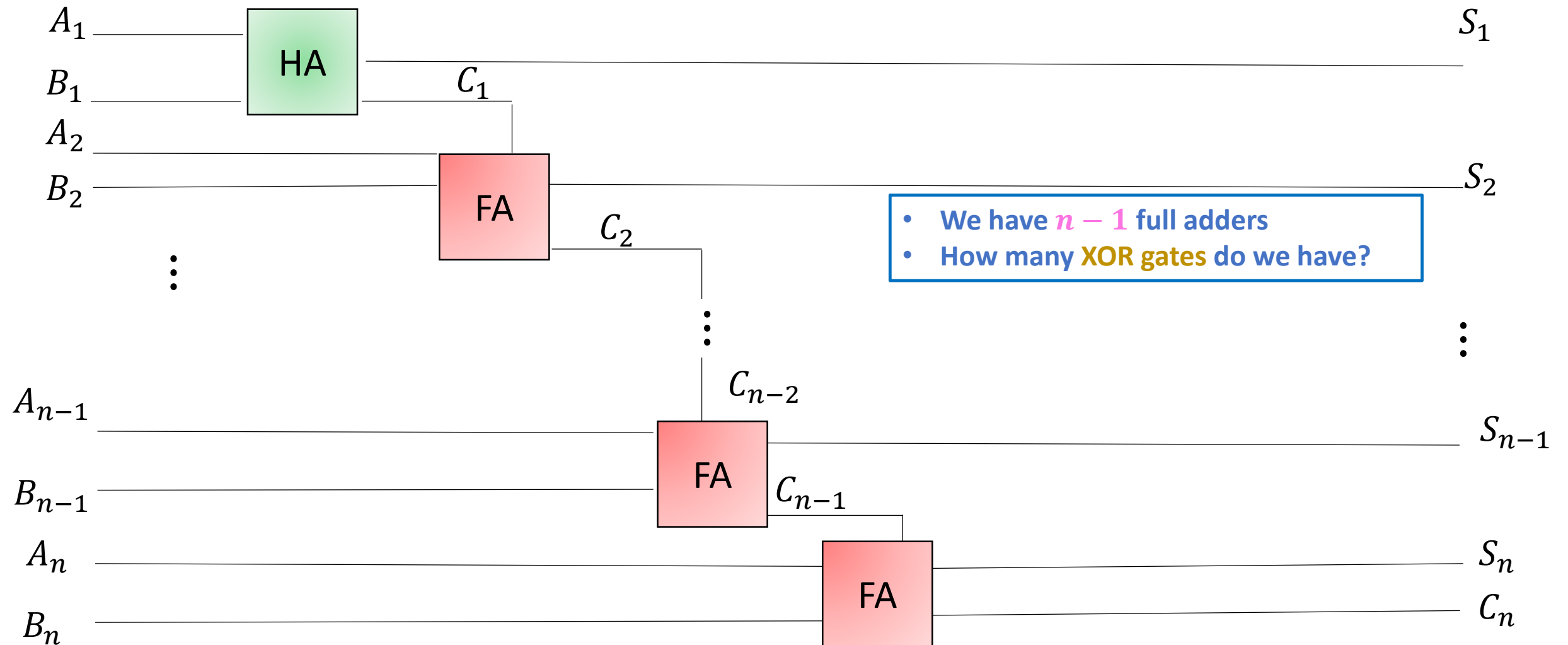

# Constructing an n-bit adder (neat)

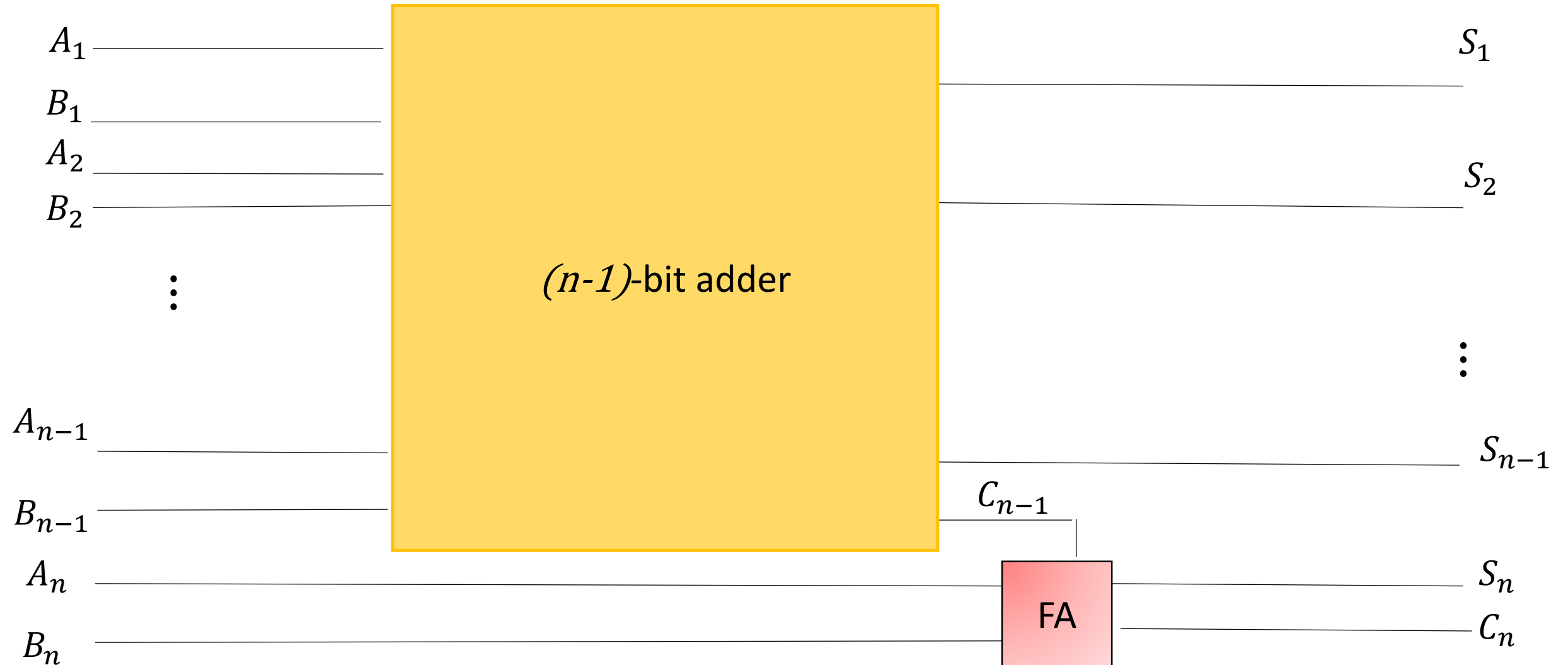


# Other numeric functions

- Addition (have done)
- Multiplication
- Division
- Primality test (test whether a number is prime)
  
- There are circuits for all of these!
  - Computers actually work this way at the base level: they consist of gates.

# Fun exercise

- Input: number in **binary**
- Output: ??? (you will tell me later)


$B_1$	$B_0$	$U_2$	$U_1$	$U_0$
0	0	0	0	0
0	1	0	0	1
1	0	0	1	1
1	1	1	1	1

 

# First micro-circuit

$B_1$	$B_0$	$U_2$	$U_1$	$U_0$
0	0	0	0	0
0	1	0	0	1
1	0	0	1	1
1	1	1	1	1

$$U_2 = B_1 \wedge B_0$$

 



## Second micro-circuit

$B_1$	$B_0$	$U_2$	$U_1$	$U_0$
0	0	0	0	0
0	1	0	0	1
1	0	0	1	1
1	1	1	1	1

$$U_1 = (B_1 \wedge \sim B_0) \vee (B_1 \wedge B_0)$$

# Second micro-circuit

$B_1$	$B_0$	$U_2$	$U_1$	$U_0$
0	0	0	0	0
0	1	0	0	1
1	0	0	1	1
1	1	1	1	1

$$U_1 = (B_1 \wedge \sim B_0) \vee (B_1 \wedge B_0) = B_1$$

*(from distributive law of conjunction over disjunction!)*



## Third micro-circuit


$B_1$	$B_0$	$U_2$	$U_1$	$U_0$
0	0	0	0	0
0	1	0	0	1
1	0	0	1	1
1	1	1	1	1

$$U_0 = (\sim B_1 \wedge B_0) \vee (B_1 \wedge \sim B_0) \vee (B_1 \wedge B_0)$$


# Third micro-circuit

$B_1$	$B_0$	$U_2$	$U_1$	$U_0$
0	0	0	0	0
0	1	0	0	1
1	0	0	1	1
1	1	1	1	1
 
$$U_0 = (\sim B_1 \wedge B_0) \vee (B_1 \wedge \sim B_0) \vee (B_1 \wedge B_0) = (\sim B_1 \wedge B_0) \vee B_1 = (\sim B_1 \vee B_1) \wedge (B_0 \vee B_1) = B_0 \vee B_1$$



# Final circuit

 

$B_1$	$B_0$	$U_2$	$U_1$	$U_0$
0	0	0	0	0
0	1	0	0	1
1	0	0	1	1
1	1	1	1	1

**STOP**

**RECORDING**